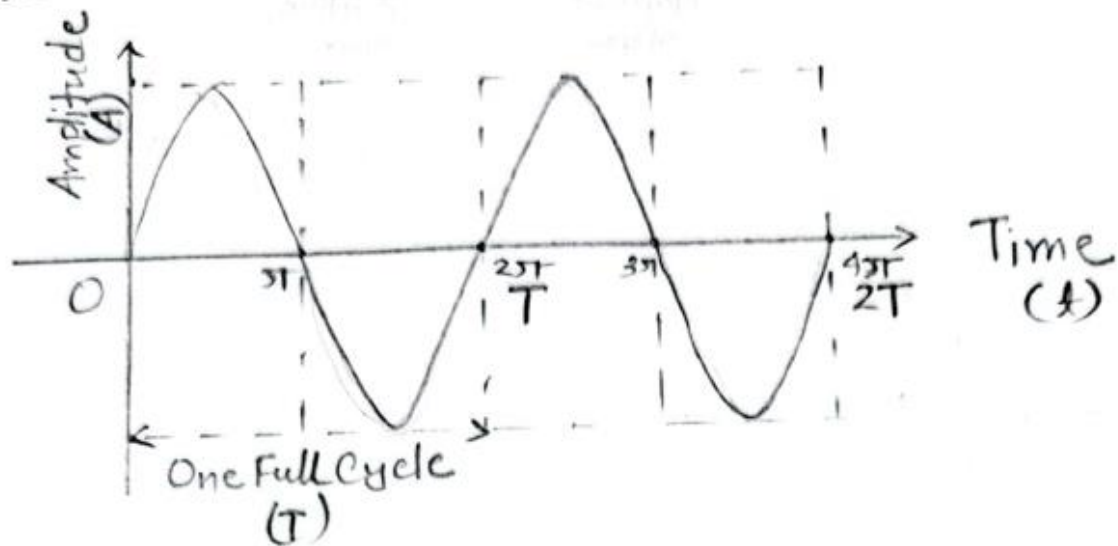


Different Types of waves:


Sin waveform:

Sine Waveform:




Square waveform:


square Waveform:

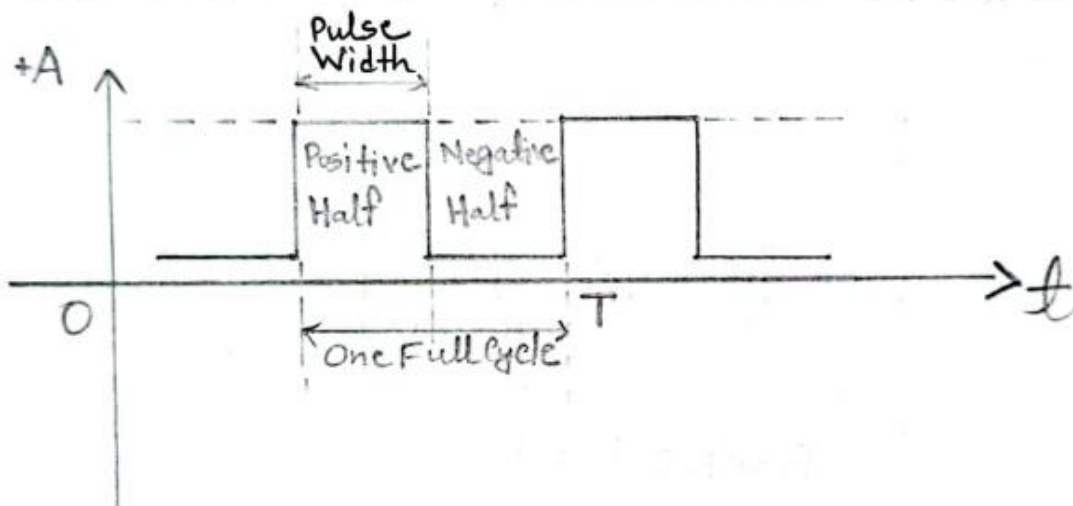


Rectangular waveform:

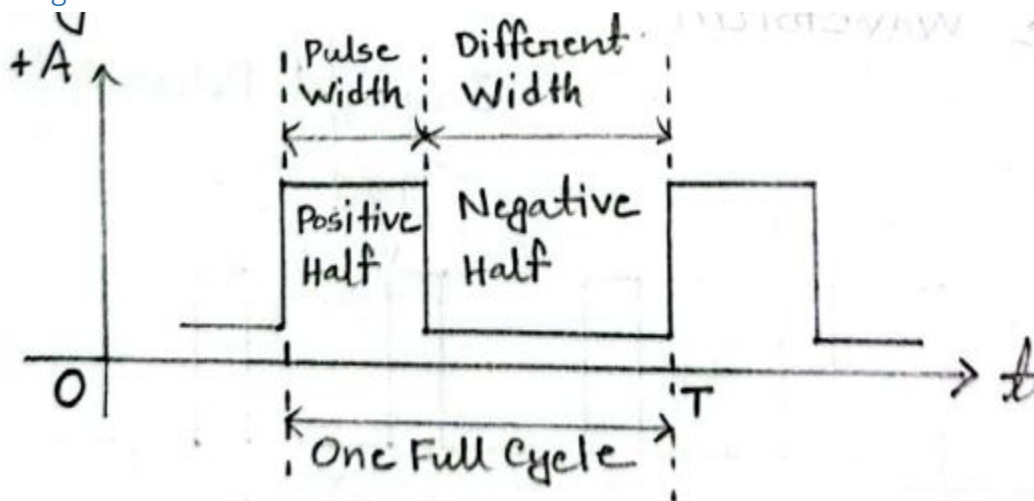


Triangular waveform:

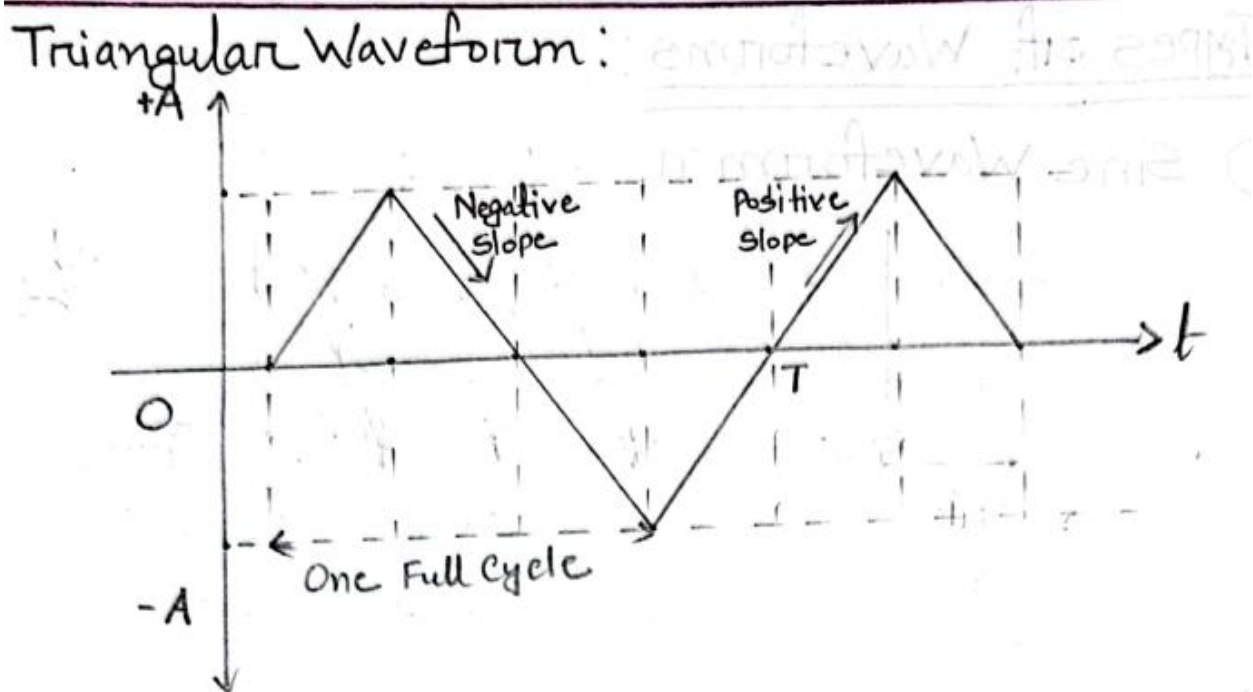


Sawtooth waveform:

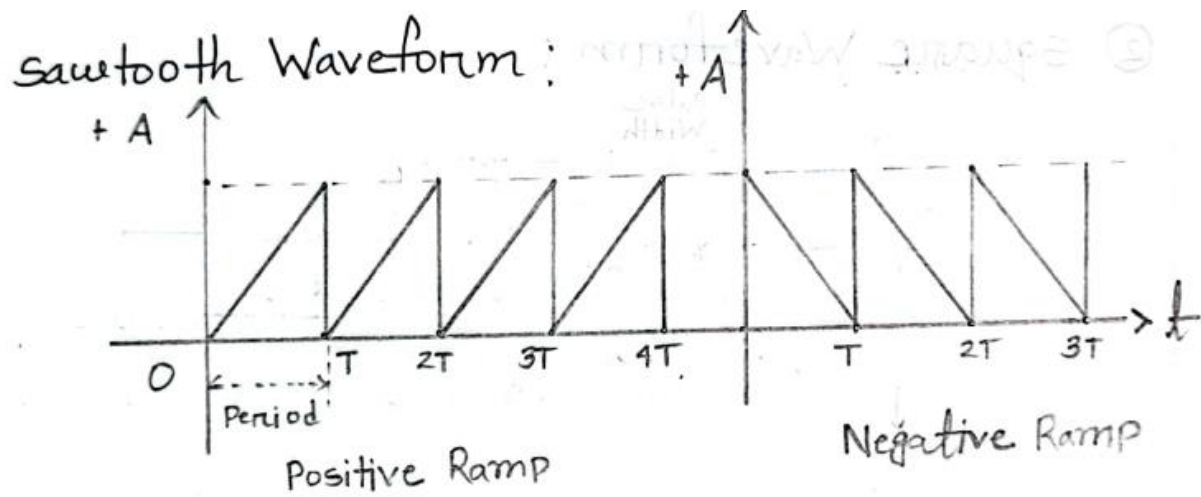


Pulse waveform:

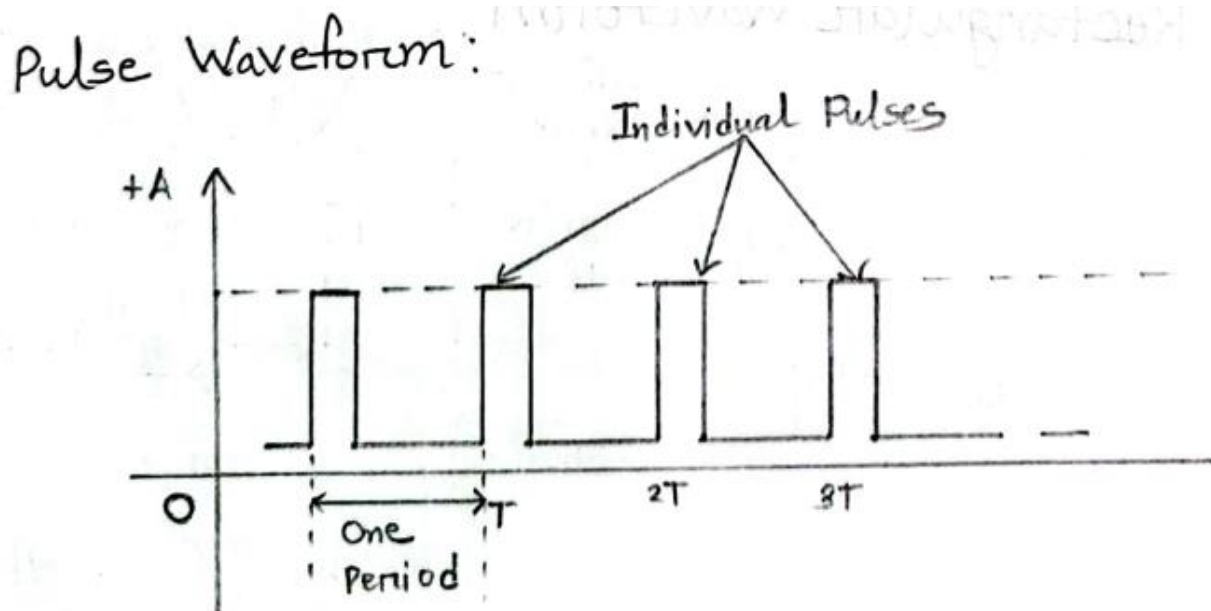

Ramp Waveform:

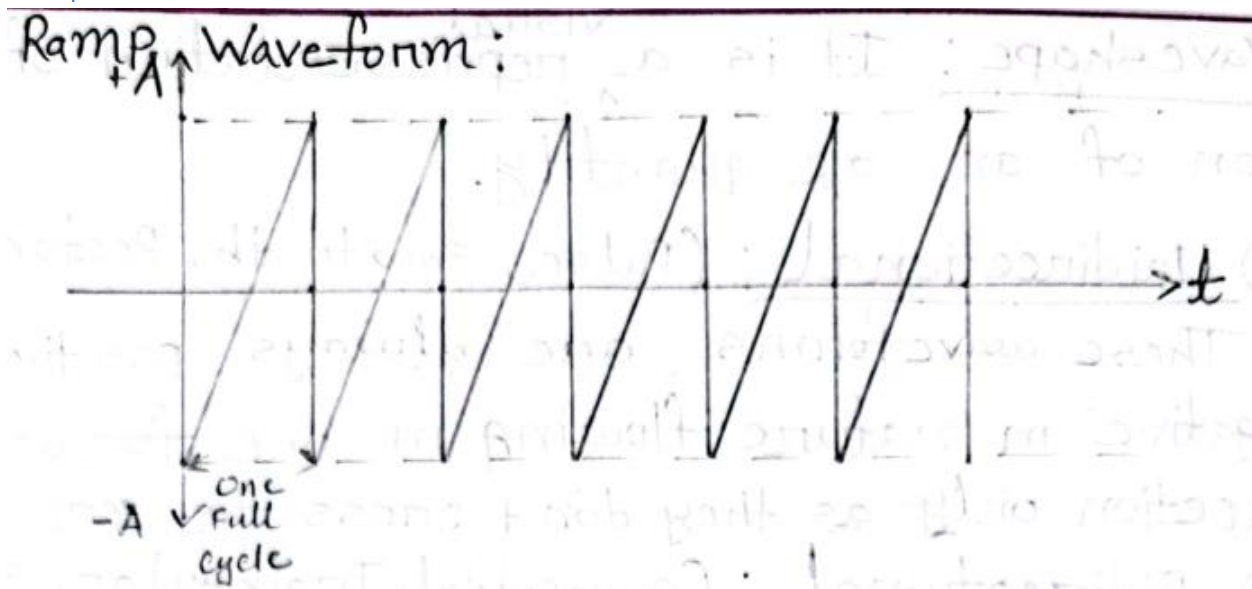

Step waveform:

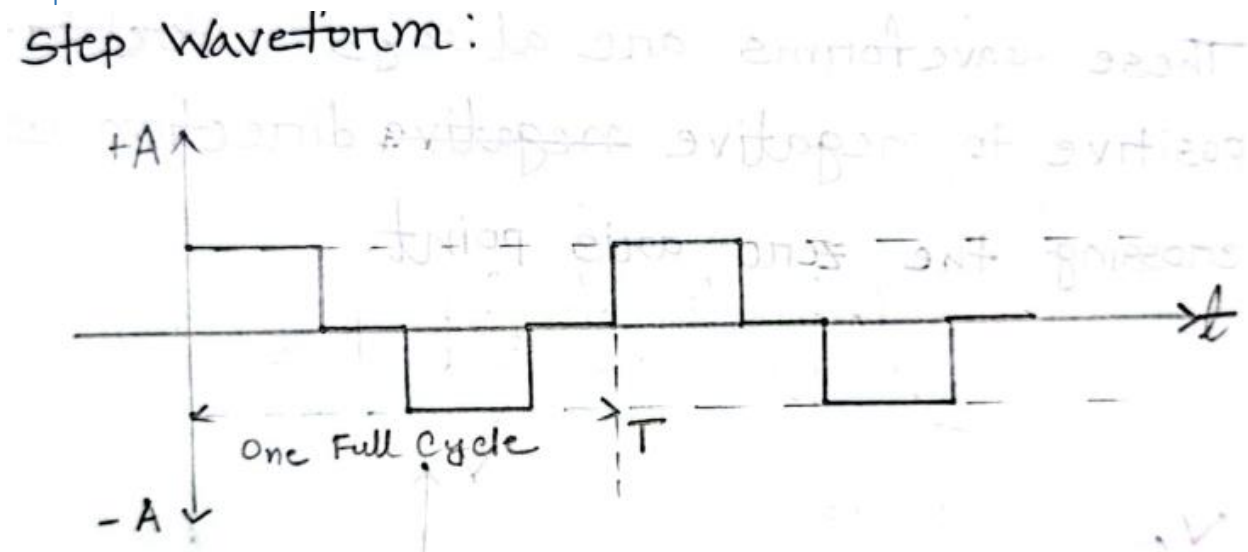

Waveshape:

Waveshape is the visual representation of variation of an AC quantity.

It's of two types:


Unidirectional:

These waveforms are either always positive or always negative, and flows in one forward direction as they don't cross the zero axis point. E.g. **pulse, sawtooth, rectangular.**

Bidirectional:

Always alters between positive and negative as they always cross the zero axis point. E.g. **Sinusoidal, Triangular, Square.**

Parts of square waveforms:

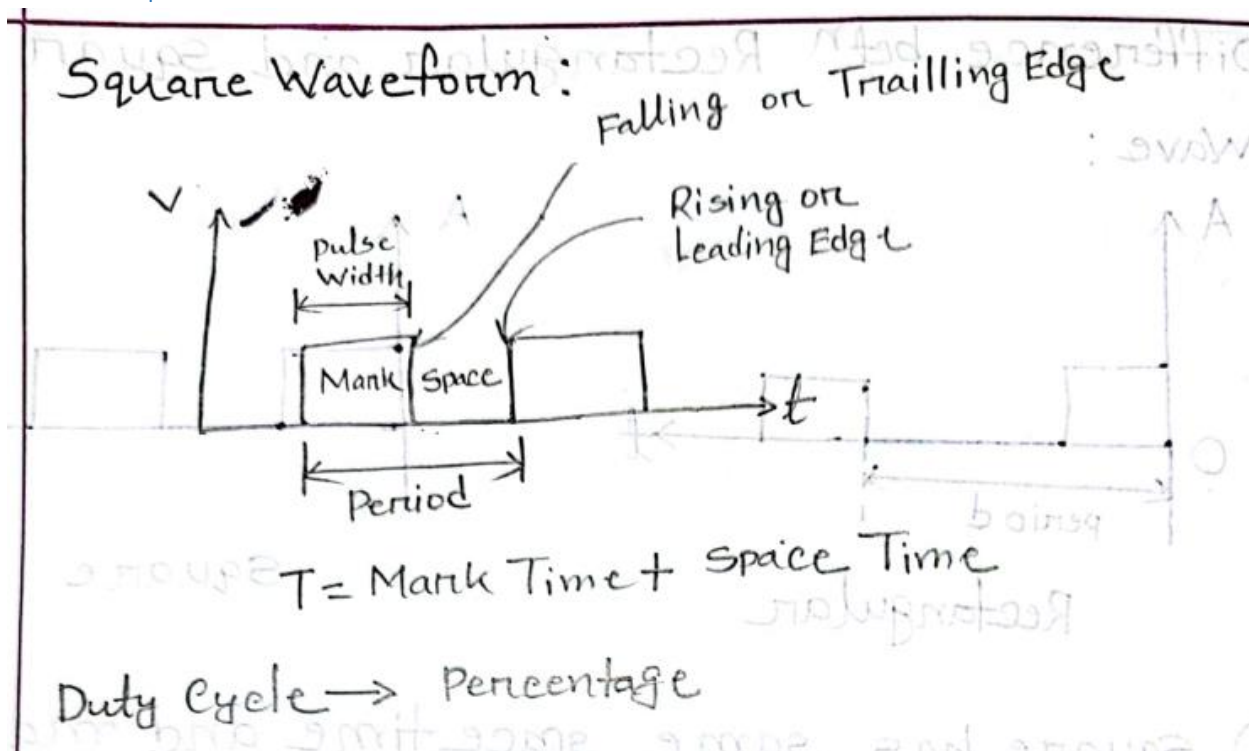

Duty cycle:

In digital circuit, the percentage of the positive pulse or mark time is called the duty cycle.

Math:

In a waveshape, the pulse width (mark time) is 20ms and duty cycle is 33%. Calculate its frequency.

20ms is 33% or 1/3rd

Solution: positive = $\tau \rightarrow 20\text{ms}$
negative = $2\tau \rightarrow 40\text{ms}$

$T = 20 + 40 = 60\text{ms}$

$f = \frac{1}{60 \times 10^{-3}} \text{ Hz} \quad (\text{Ans.})$


Difference between Rectangular and square waves:

- Square has same space and mark time, thus 50% duty cycle.
- Square is symmetrical.
- Square is used in electronics and micro electronic devices. Used to generate clock signals and timing circuits.

- Rectangular wave is used for varying any electrical quantity by varying the power supplied to a load.


Step waveshape:

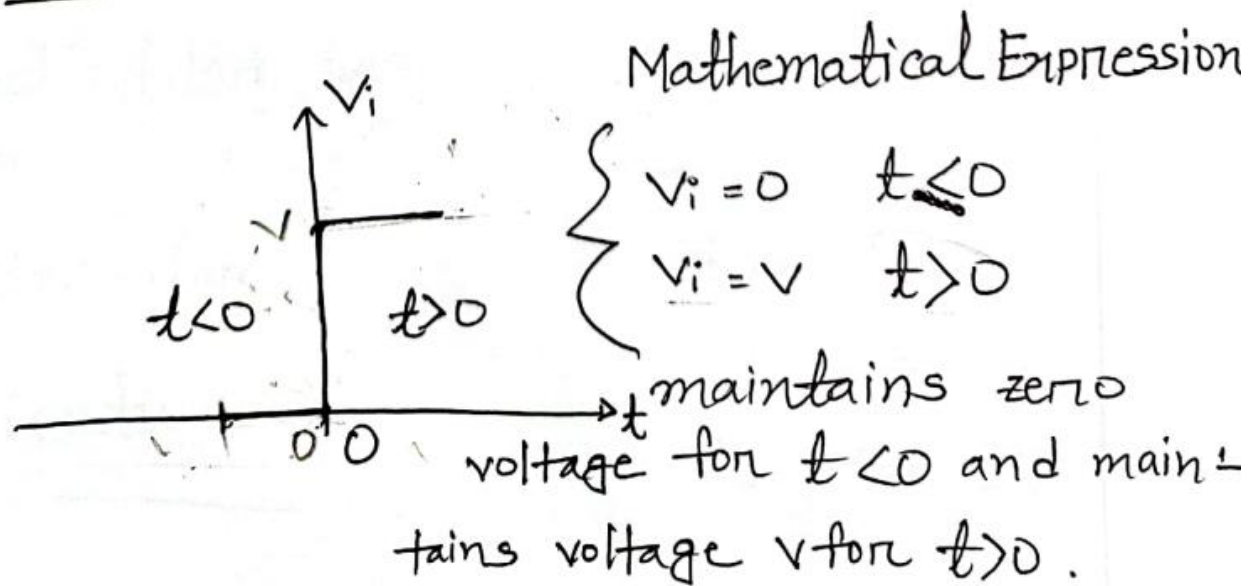A step voltage is one which maintains voltage 0 when $t < 0$ and voltage v when $t > 0$.



Ramp waveshape:

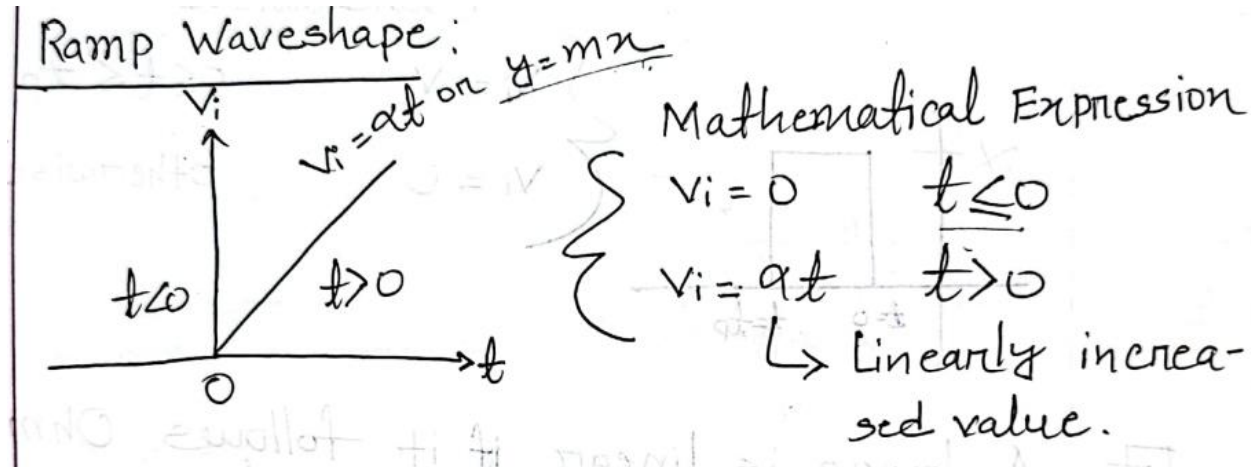
A ramp voltage is one where voltage 0 is maintained when $t \leq 0$ and voltage linearly increased when $t > 0$.



Pulse waveshape:


A pulse voltage is when voltage is maintained at v when $0 \leq t \leq t_p$, otherwise maintained at $v=0$.

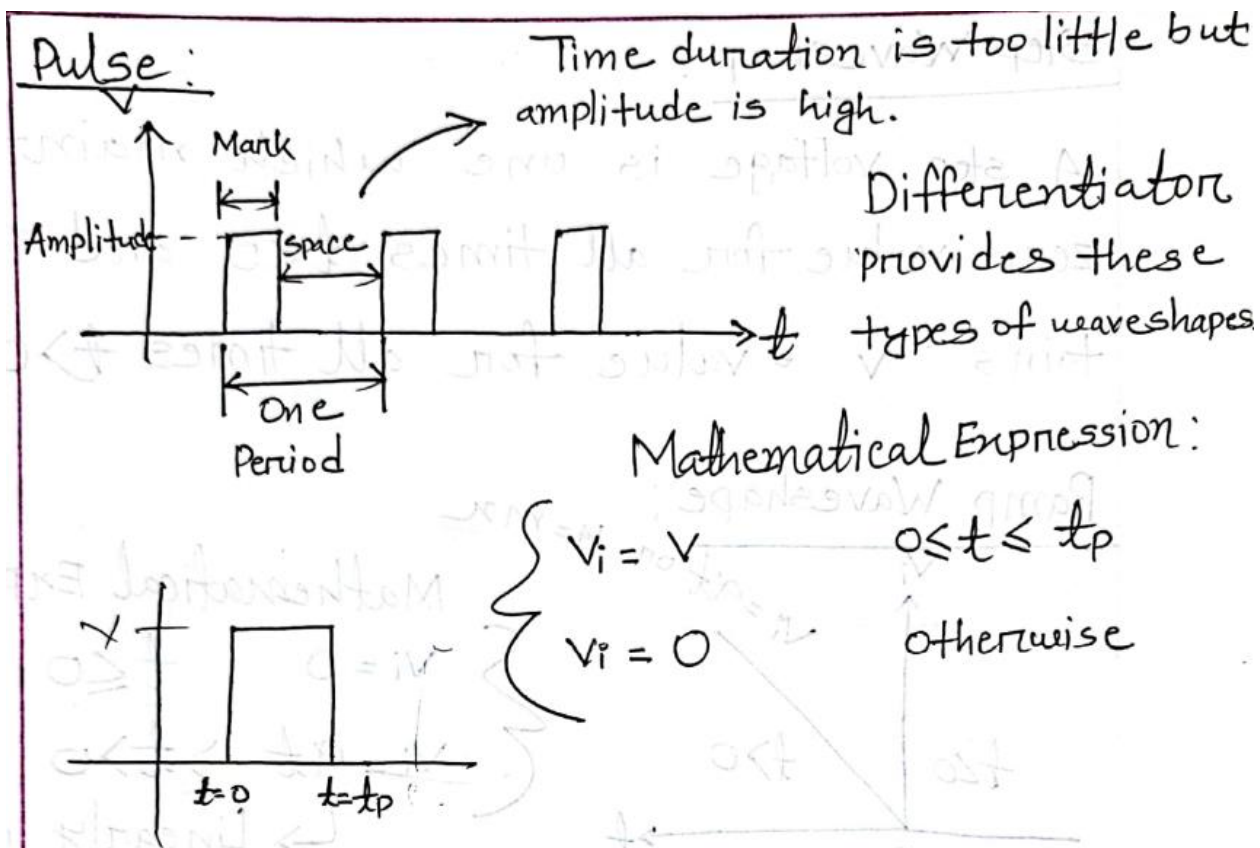Here time duration is too small for mark, but amplitude is high.




V-I characteristics:

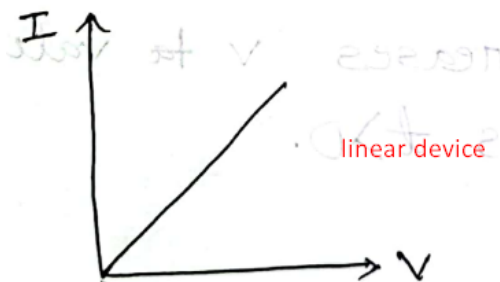A device is linear when it follows ohm's law i.e. R, L, C.



Diode and transistors are nonlinear devices:

Diode V-I characteristic:

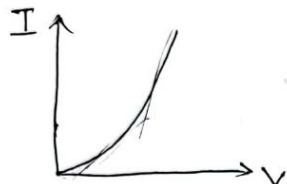

Linear waveshaping:

Linear elements such as resistors, capacitors and inductors are employed to shape a signal in this linear wave shaping.

Filtering:

Filtering is the process where unwanted portion of a signal is removed.



1. Low pass filter
2. High pass filter

Capacitive reactance:


Capacitor blocks DC current. In DC, frequency is zero, thus reactance is infinite, thus blocking it. For AC, the higher the frequency or f , lower reactance, thus letting higher frequencies pass and blocking low frequencies.

$$X_c = \frac{1}{2\pi f C}$$

Here:

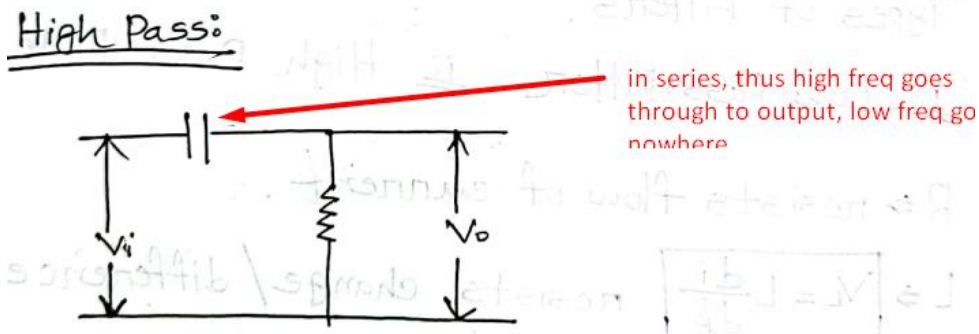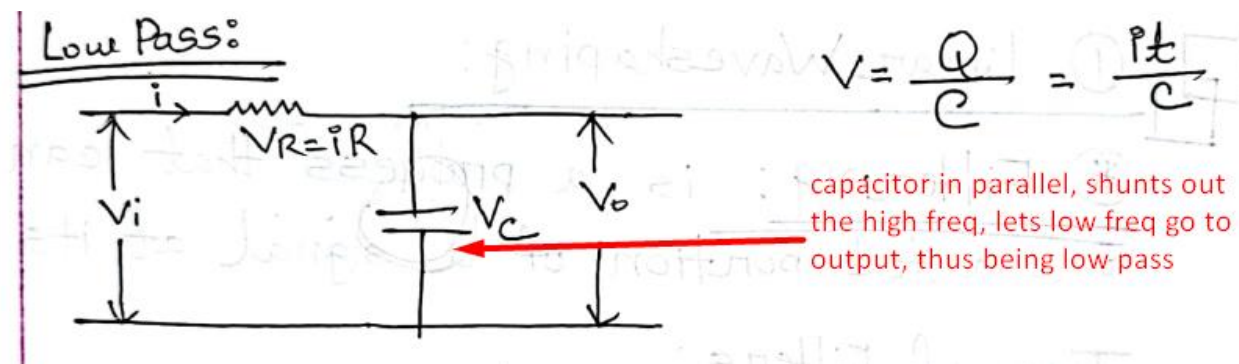

Low pass filter as integrator:

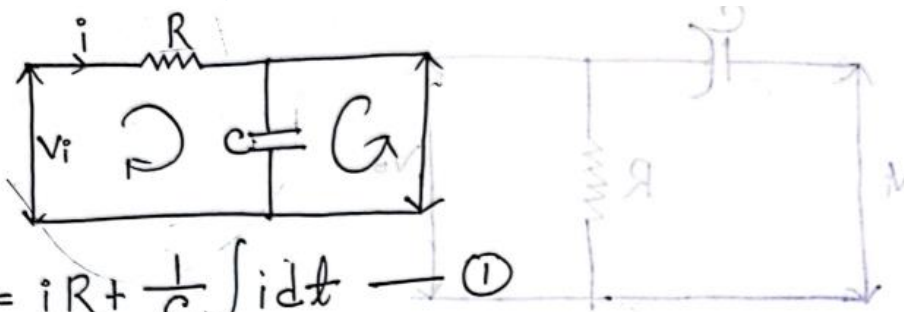

$$V_i = iR + \frac{1}{C} \int i dt \quad \text{--- (1)}$$

$$V_o = \frac{1}{C} \int i dt \quad \text{--- (2)}$$

since, $\frac{1}{C} \int i dt \ll iR$

low pass, so DC is way higher
iR represents DC

from (1)

$$V_i = iR$$

$$\Rightarrow i = \frac{V_i}{R}$$


$$\text{(2) } V_o = \frac{1}{C} \int i dt$$

$$= \frac{1}{C} \int \frac{V_i}{R} dt$$

$$\therefore V_o = \frac{1}{RC} \int V_i dt$$

$\therefore V_o \propto \int V_i dt$ as $\frac{1}{RC}$ is constant.

High pass filter as differentiator:

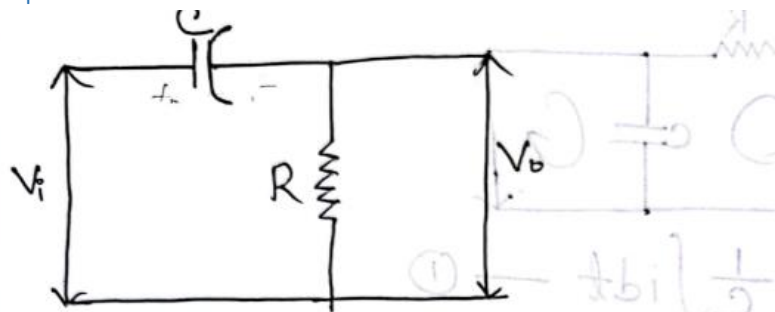

$$V_i = \frac{1}{C} \int i dt + iR \quad \text{--- (1)}$$

$$V_o = iR \quad \text{--- (2)}$$

since, $iR \ll \frac{1}{C} \int i dt$

$$\text{From (2)} \Rightarrow i = \frac{V_o}{R}$$

From (1) \Rightarrow

$$\begin{aligned} V_i &= \frac{1}{C} \int i dt \\ &= \frac{1}{C} \int \frac{V_o}{R} dt \end{aligned}$$

$$V_i = \frac{1}{RC} \int V_o dt$$

differentiating both sides,

$$\frac{dV_i}{dt} = \frac{V_o}{RC}$$

$$\text{or, } V_o = RC \frac{dV_i}{dt}$$

$$\therefore V_o \propto \frac{dV_i}{dt} \text{ as } RC \text{ is constant.}$$


Sinusoidal input to a High pass filter:

Cut off frequency:

This "Cut-off", "Corner" or "Breakpoint" frequency is defined as being the frequency point where the capacitive reactance and resistance are equal. Capacitive resistance increases with frequency.

$$f_c = \frac{1}{2\pi RC}$$

Calculation:

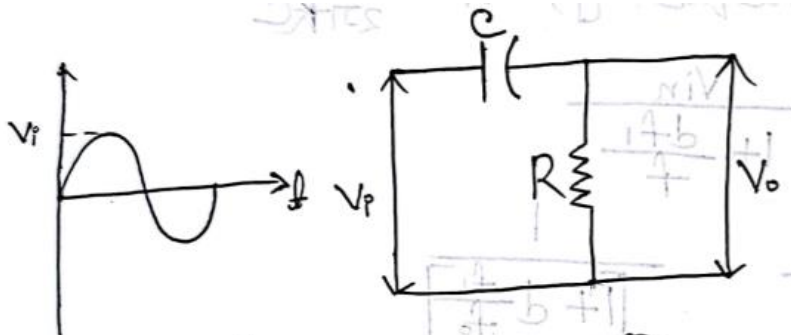

$i = \frac{V}{Z} \rightarrow \text{impedance}$
 $= \frac{V}{R + dX_c}$
 where $X_c = \frac{1}{2\pi fC}$
 $d = \text{complex const } i$

$$V_i = \frac{1}{C} \int i dt + iR \quad \text{--- (1)}$$

$$V_o = iR \quad \text{--- (1)}$$

$$\therefore i = \frac{V_{in}}{R + d \cdot \frac{1}{2\pi fC}} = \frac{V_{in}}{R \left[1 + \frac{d}{2\pi fCR} \right]} \quad \text{--- (2)}$$

From ① \Rightarrow

$$V_o = \frac{V_{in}}{R \left[1 + \frac{d}{2\pi f C R} \right]} R$$

$$\text{or, } V_o = \frac{V_{in}}{1 + \frac{d}{2\pi f R C}}$$

$$X_c = \frac{1}{2\pi f C}$$

$$f = \frac{1}{2\pi X_c C}$$

Let;

$$\text{cut off frequency, } f_1 = \frac{1}{2\pi R C}$$

$$\text{or, } V_o = \frac{V_{in}}{1 + \frac{d f_1}{f}}$$


$$A = \frac{V_o}{V_{in}} = \frac{1}{1 + d \frac{f_1}{f_0}}$$

$$|A| = \frac{1}{\sqrt{1 + \left(\frac{f_1}{f_0} \right)^2}}$$

$$\theta = \tan^{-1} \left(\frac{f_1}{f} \right)$$

it is being calculated in
complex plane

Amplitude

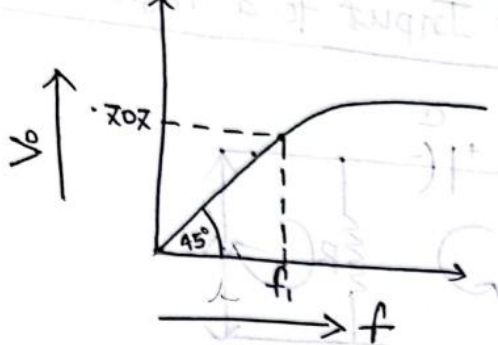

some such we will find one frequency point for which $f_1 = f$.

When $f_1 = f$,

$$\text{Amplitude} = \frac{1}{\sqrt{1+(1)^2}} = \frac{1}{\sqrt{2}} = 0.707$$

$$\theta = \tan^{-1}(1) = 45^\circ$$

The point where $f_1 = f$ is called 3dB point

Step input to a high pass filter:

Step input is when for $t > 0$ $V_{in} = v$ and $t < 0$ $V_{in} = 0$.

The transition between two voltage occurs at $t=0$

$$V_i = 0 \text{ when } t = 0^-$$

$$V_i = V \text{ when } t = 0^+$$

$$V_i = \frac{1}{C} \int i dt + iR \quad \text{--- (1)}$$

$$V_o = iR \text{ (2)} \Rightarrow i = \frac{V_o}{R} \quad \text{--- (2)}$$

From ① \Rightarrow

$$V_i = \frac{1}{C} \int \frac{V_o}{R} dt + \frac{V_o}{R} \cdot R$$
$$= \frac{1}{RC} \int V_o dt + V_o$$

Differentiating both sides

$$\frac{dV_i}{dt} = \left(\frac{1}{RC} \times V_o \right) + \frac{dV_o}{dt}$$

steady state response transient state

constant value

③

If $V_i = V$ [V is a constant]

$$\frac{dV_i}{dt} = \frac{dV}{dt} = 0$$

④

From ③ \Rightarrow

$$\frac{1}{RC} V_o + \frac{dV_o}{dt} = 0 \longrightarrow \text{Differential Eqn}$$

The general solution will be,

$V_o =$ complementary function + particular integral — ⑤

Complementary Equation :

$$\frac{dV_i}{dt} = \frac{V_o}{RC} + \frac{d}{dt} V_o \quad \text{--- (6)}$$

Let us consider,

$$D = \frac{d}{dt}$$

Then (6) is,

$$DV_i = \frac{V_o}{RC} + DV_o$$

or, $DV_i = V_o \left(D + \frac{1}{RC} \right)$

L.H.S. ... R.H.S.

To find complementary function,

$$V_o \left[D + \frac{1}{RC} \right] = 0$$

$$\Rightarrow D = - \frac{1}{RC}$$

Complementary Function = $k e^{+ \phi t}$

$$= k \cdot e^{- \frac{t}{RC}}$$

Particular Integral:

DV_i
 $\Rightarrow \frac{d}{dt} V = 0$


\therefore Particular Integral = 0

From (5) \Rightarrow


$$V_o = \left(k e^{- \frac{t}{RC}} + 0 \right) \text{ (exponential curve)}$$

\rightarrow we don't know the value of "k" yet.

Curve will degrade from k value.

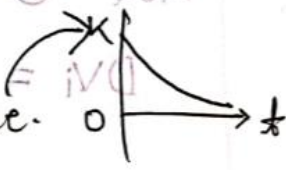


$$V_0 = V e^{-t/RC}$$

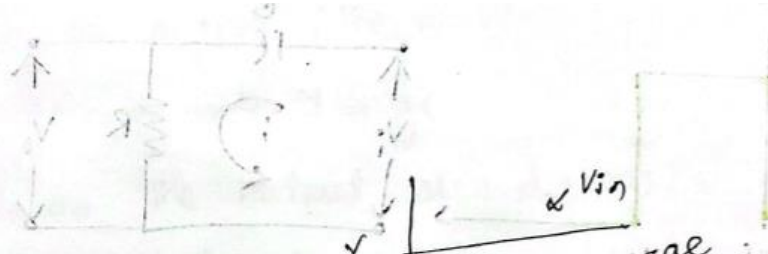

i) At $t = RC$

$$V_0 = V e^{-RC/RC} = 0.3678V$$

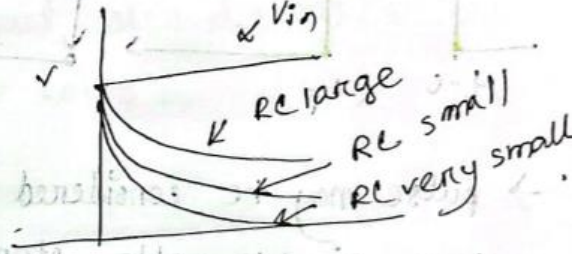

ii) At $t = 2RC$

$$V_0 = V e^{-2RC/RC} = 0.135V$$

iii) At $t = 3RC$

$$V_0 = V e^{-3RC/RC} = 0.049V$$

iv) At $t = 5RC$

$$V_0 = V e^{-5RC/RC} = 0.007V$$

\therefore The output voltage V_0 becomes practically zero after 5 time-constants.


Pulse waveform as input to a HPF:

May be considered as the sum of two step wave, $+v$ when $t=0$ and $-v$ when $t=t_p$.

There are three situations to this output:

For ① If the pulse is applied to the High Pass Filter, the response for time $t < t_p$ is same as step voltage input.

$$V_p = V_o = V e^{-\frac{t_p}{RC}}$$

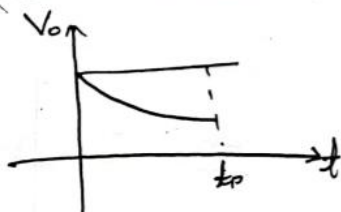

where $t < t_p$

② At the end of the pulse, the input falls quickly by the amount V .


So, the output voltage also decreases by the same amount V .

At $t = t_p$, $V_o = V_p - V$

where $t = t_p$

$$\text{or, } V_o = V e^{-\frac{t_p}{RC}} - V$$

$$= V [e^{-\frac{t_p}{RC}} - 1]$$

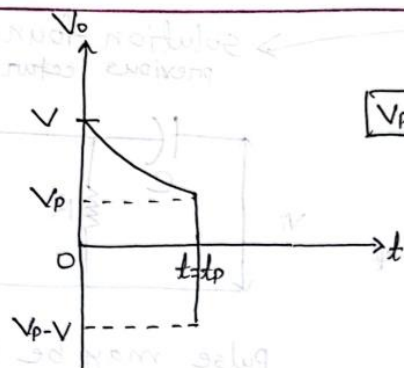


$$V_p - V$$


③ $t = t_p^+$ on $t > t_p$

$$V_o = (V_p - V) e^{-\frac{(t-t_p)}{RC}}$$
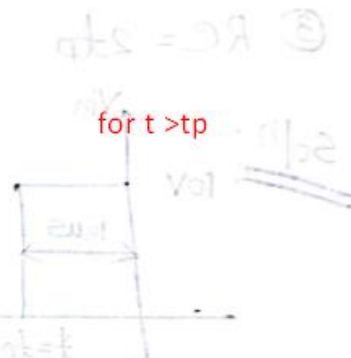
$$= (V e^{-\frac{t_p}{RC}} - V) e^{-\frac{t-t_p}{RC}}$$



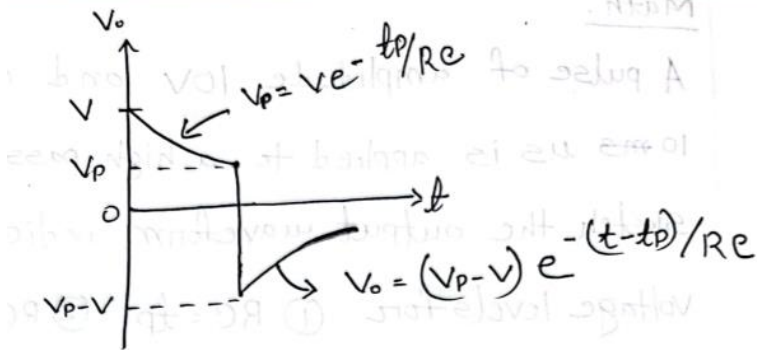If we know t_p , V_p and $V_p - V$ then we can draw the curve




If we know t_p , V_p , and $V_p - V$ then we can draw the curve.

MATH:

A pulse of amplitude 10V and duration 10 μ s is applied to a high pass filter. sketch the output waveform indicating the voltage levels for ① $RC = t_p$ ② $RC = 0.5 t_p$

③ $RC = 2 t_p$

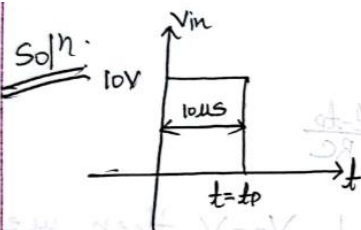


Input
Waveshape

① When $RC = t_p = 10 \mu s$

$$V_p = V e^{-\frac{t_p}{RC}} = 10 \cdot e^{-1} = 3.68 \text{ V}$$

$$V_p - V = 3.68 - 10 = -6.32$$

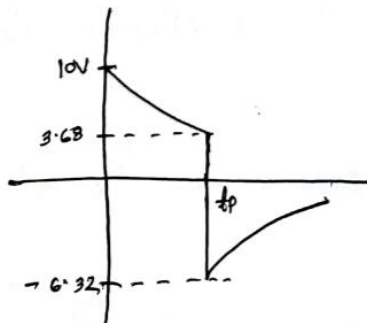


Output
Waveshape

② When $RC = 0.5 t_p$

$$V_p = V e^{-\frac{t_p}{RC}} = 10 \cdot e^{-2} = 1.35$$

$$V_p - V = 1.35 - 10 = -8.65$$

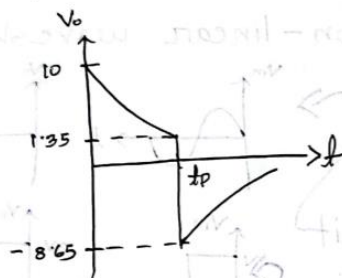

Output Waveshape

Nonlinear waveshaping:

The circuits where the output waves are non-sinusoidal for sinusoidal input, are called non-linear waveshaping.

1. Clipper
2. Clamper

Application of clipper circuit:


1. For shaping of the wave
2. For removing noise peak
3. For limiting the magnitude of voltage

Application of clamper:


1. Can be used as voltage doubler
2. Used in SONAR and RADAR
3. Used in TV as voltage stabilizer
4. Used for removing distortion

Clipper:

Classifications:

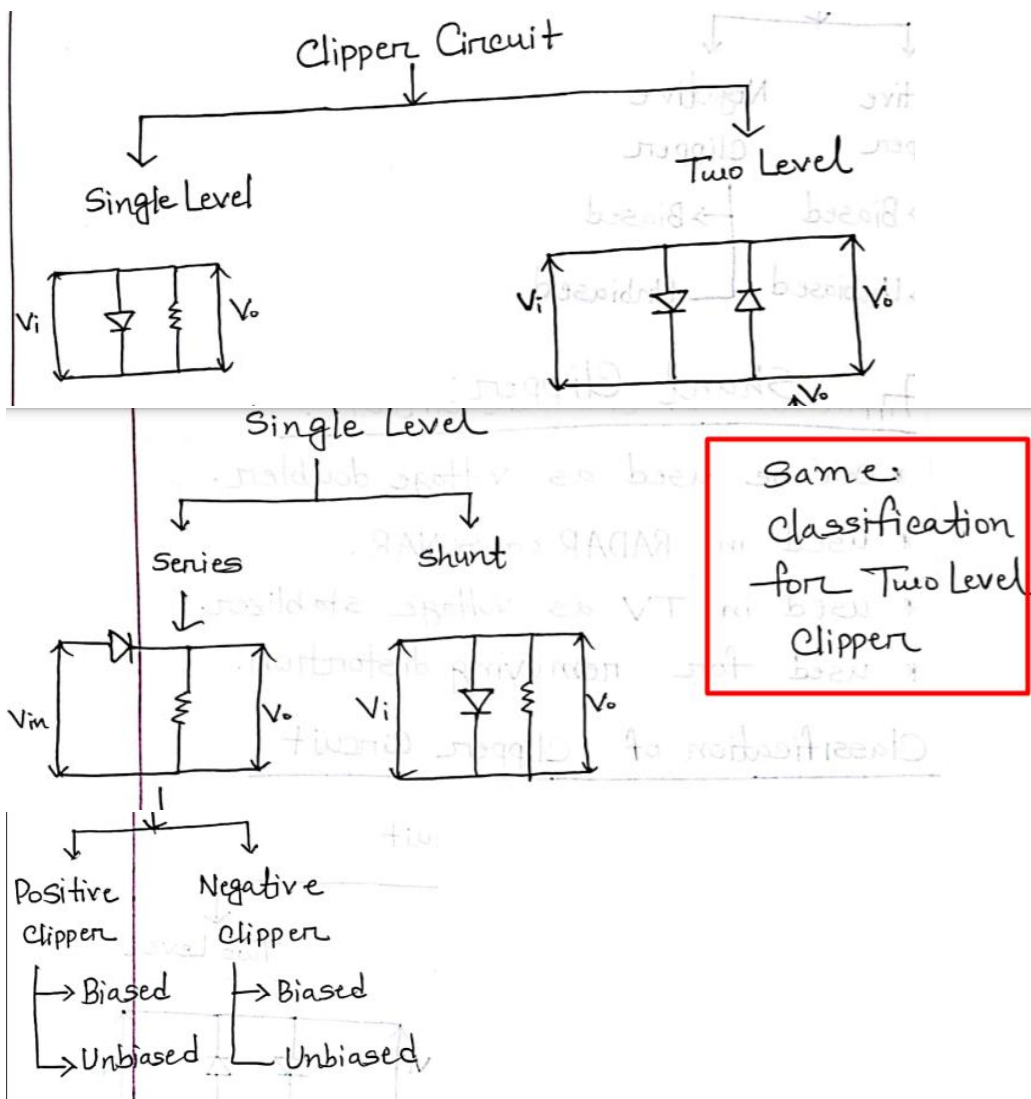


EXAMPLE:

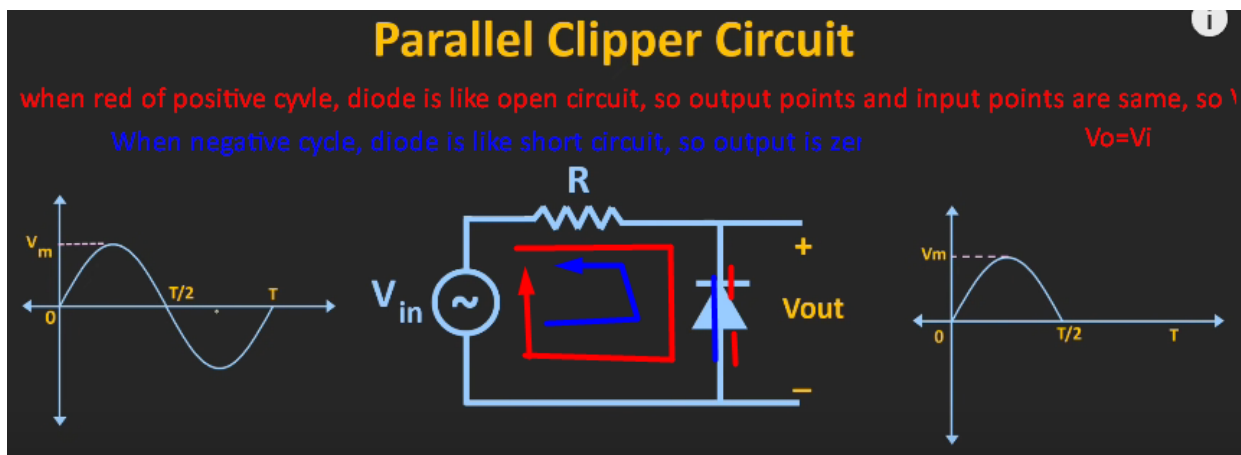

If diode voltage is given, when in forward bias, there will be a voltage drop, so output will not be exact zero, it will be $-V_d$.

Clipper Circuit with Biasing Voltage

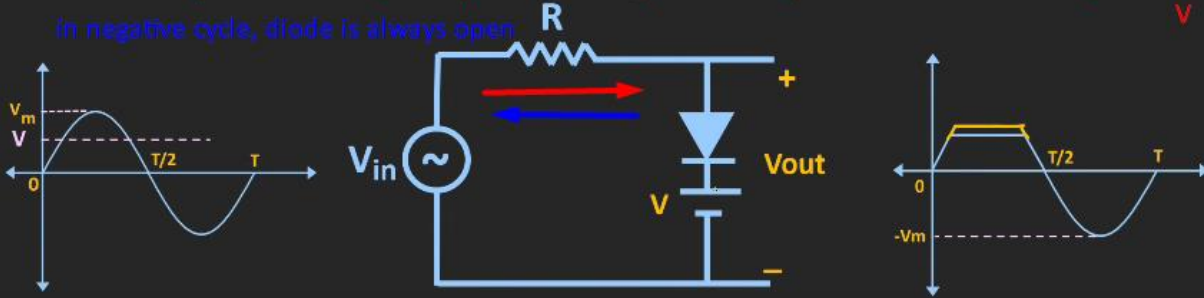
when V_{in} keeps forward bias, V keeps reverse bias, until $V_{in} > V$, after that diode is short, so V_o is V
 in negative cycle, diode is always open



While biasing in clipper, the V is always makes the diode reverse biased if waveshape is on axis.


Here is **Negative biased clipper**:

Clipper Circuit with Biasing Voltage

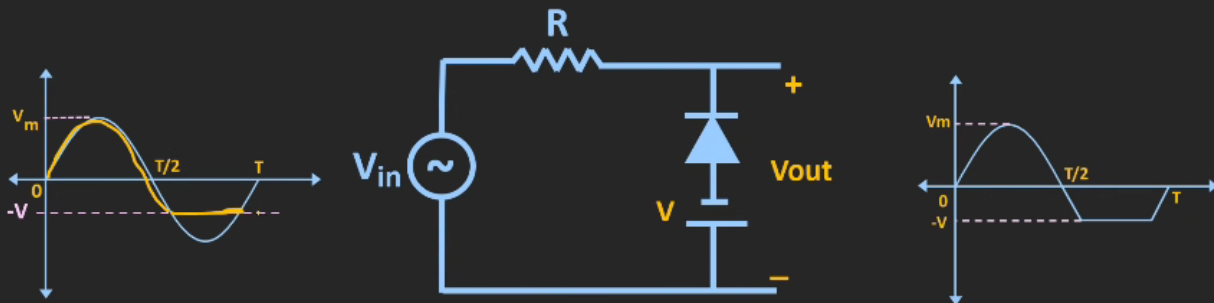

Two ways:

Clipper Circuit with Biasing Voltage

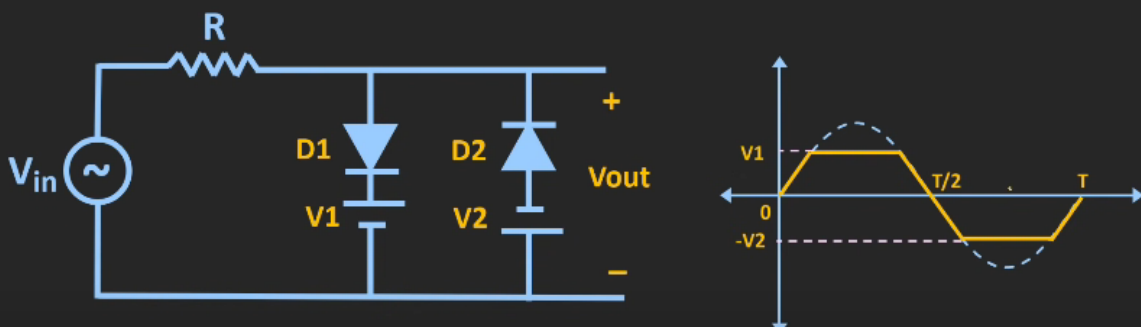


In positive cycle, $D1$ is shorted after $V_{in} > V1$, $D2$ is always open. Vice versa for negative cycle


Series Clippers:

Are simple, one cycle goes other doesn't.

Series Clipper Circuit


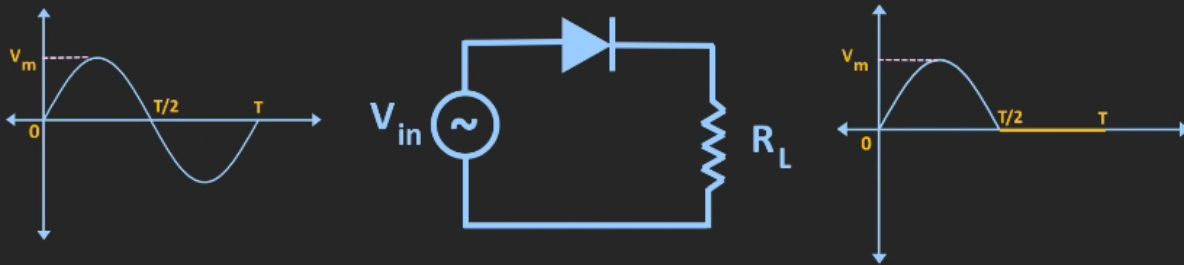


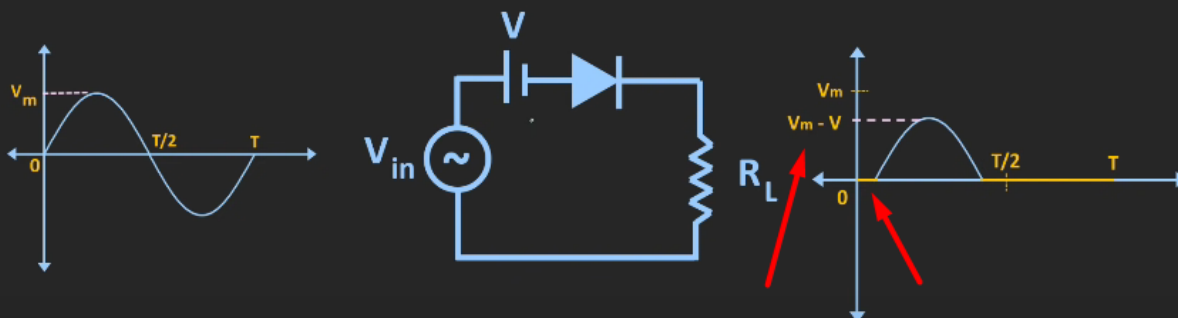Series Clipper Circuit with Biasing Voltage



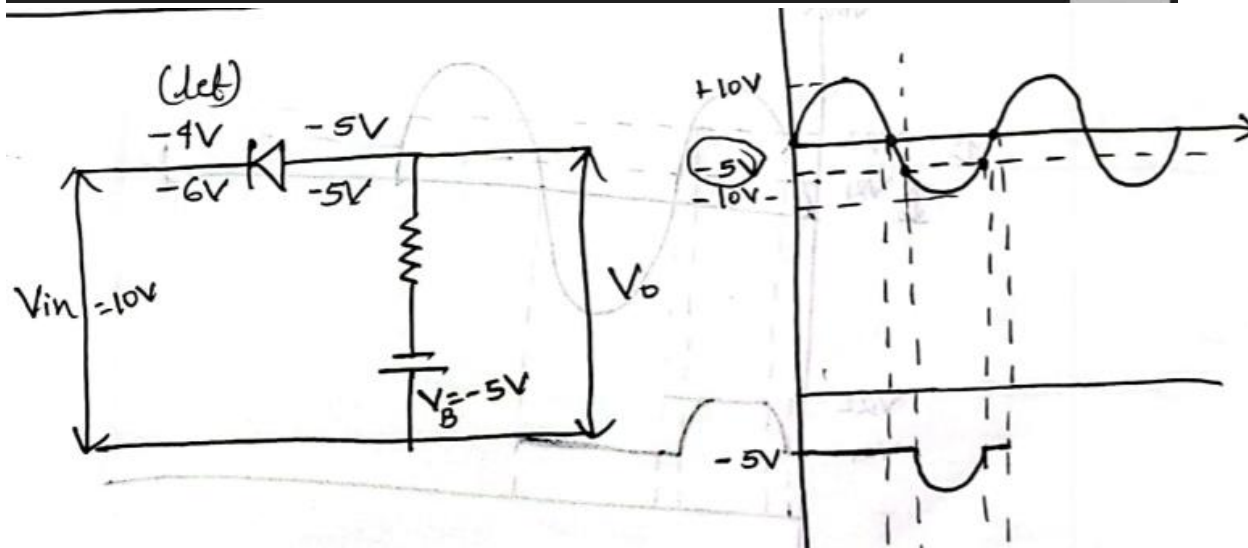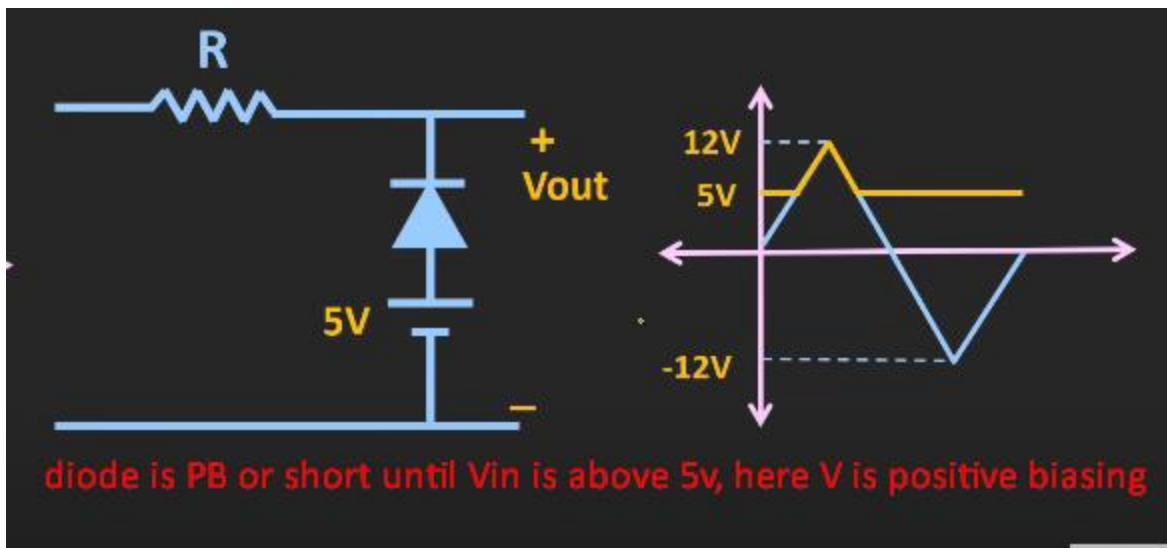in positive cycle, diode isn't forward biased until $V_{in} > V$, and when short, there is a V voltage dro






Here output is always -5v until there is a higher voltage source, meaning, when $V_{in} < -5v$

Clamper:


A clamping circuit is one which takes an input waveform and provides a faithful replica of its shape, but has one edge tightly clamped to zero voltage reference point.

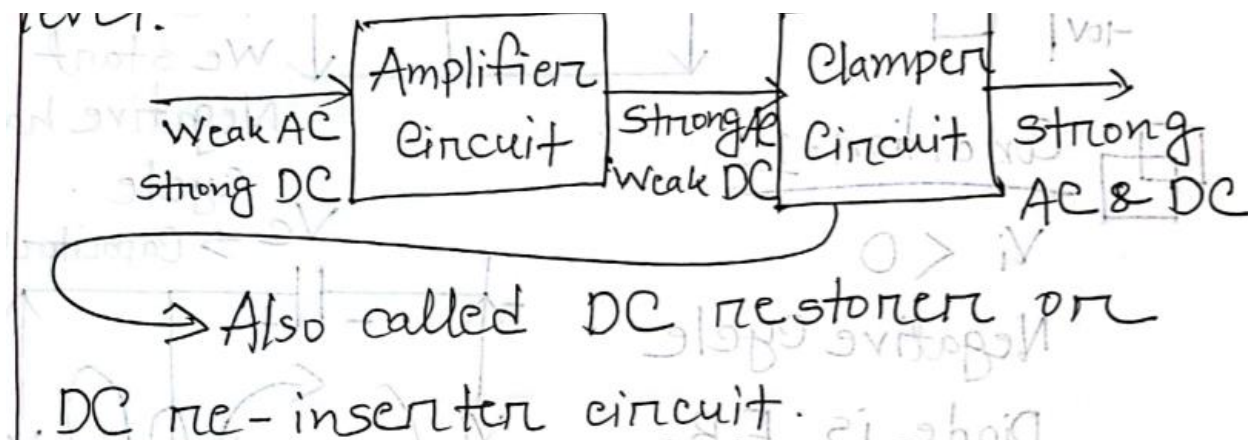Why use: Clamping is used to introduce a DC component to a signal after going through a capacitor coupling.



EXAMPLE:


Negative Clamper Circuit

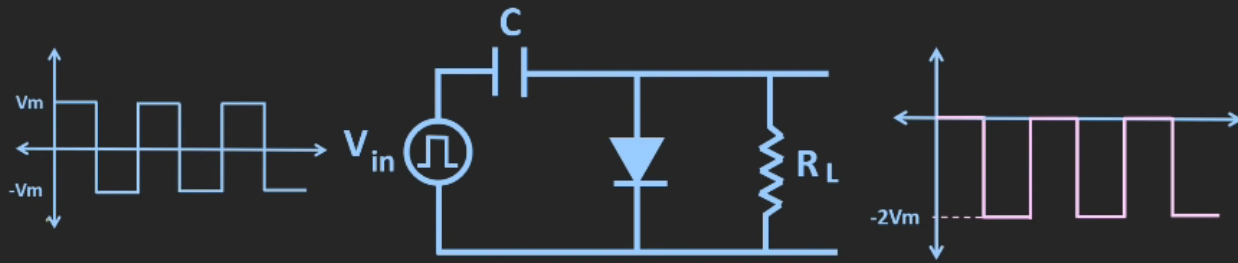

In positive cycle, diode is shorted, so output is zero. C is charged to V_m .

In negative cycle, diode is open, so output is input + capacitor discharge, meaning $2V_m$


Clamper Circuit with Biasing Voltage

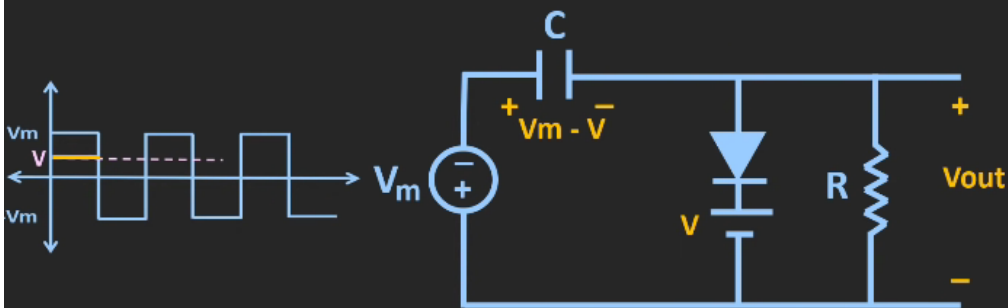


Here, the capacitor is charged to $V_m - V$ in positive half cycle, and diode is shorted, so output is V . In negative half, diode is open. So output is input + discharge. So $-2V_m + V$.

Calculation is given below.

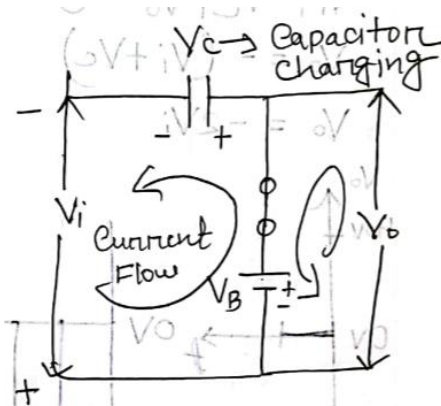
Condition - 1:
 $V_i < 0$
 Negative cycle
 Diode is F.B.
 so, act as short circuit
 $V_o = V_B$
 Apply KVL,
 $-V_i - V_B + V_C = 0$
 $V_C = V_i + V_B$



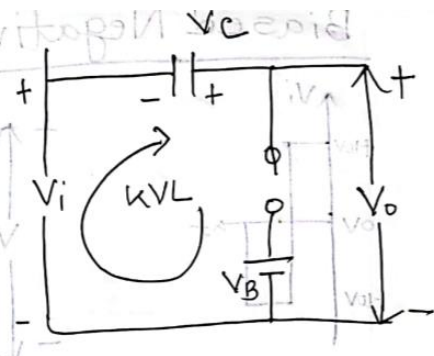Condition - 2:
 $V_i > 0$
 Positive cycle
 Diode is R.B.
 so, act as open circuit



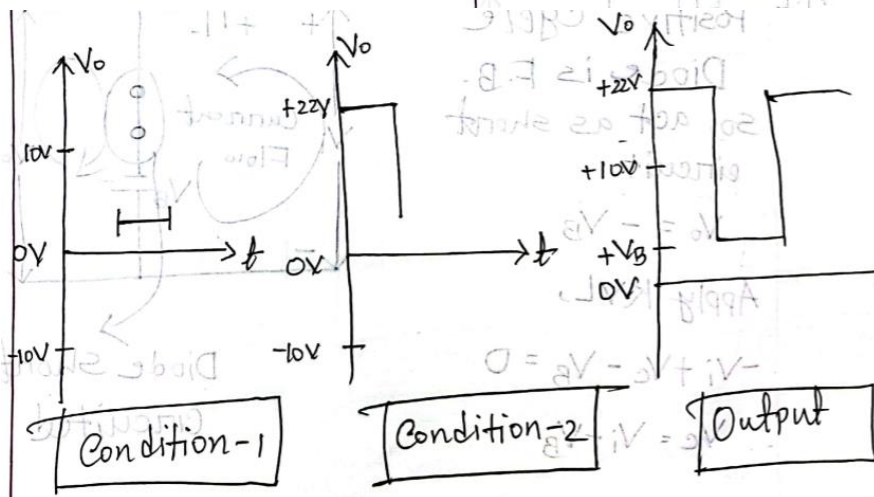Apply KVL,
 $-V_i - V_C + V_o = 0$
 or, $V_o = V_i + V_C$
 $\therefore V_o = 2V_i + V_B$



Switching circuit:

A circuit which can turn on or off in an electrical circuit is known as a switching circuit.

Has two parts:

1. A switch:
 - a. Mechanical switch
 - b. Electro-mechanical switch

c. Electronic switch

2. Associated circuitry

Characteristics of different switches:

Electro-mechanical switch:

A mechanical switch that is operated electrically.

Pros:

- Requires very small amount of current
- Can turn on or off from a distance
- No danger of sparking

Cons:

- Has moving parts, thus has friction
- Less than 5 operations per second at maximum.

Electrical switches:

Switches that can turn on or off electrically with help of diode, transistors etc.

Pros:

- Cheaper and smaller
- No noise and friction
- 10^9 operations per second
- Trouble free service because of solid state

Diode as switching device:


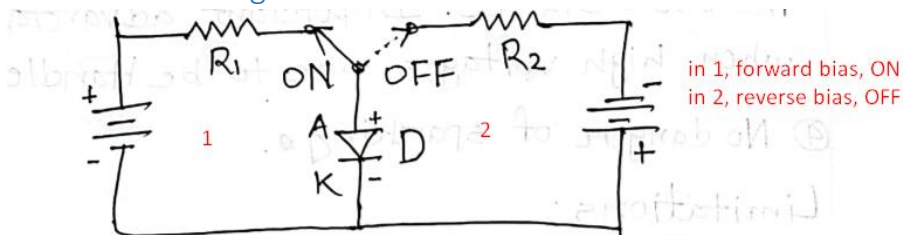


Fig: switching circuit using diode.

If,


- The majority carriers in P-type holes = P_{po}
- The majority carriers in N-type electrons = N_{no}
- The minority carriers in P-type electrons = N_{po}
- The majority carriers in N-type holes = P_{no}

During forward bias:

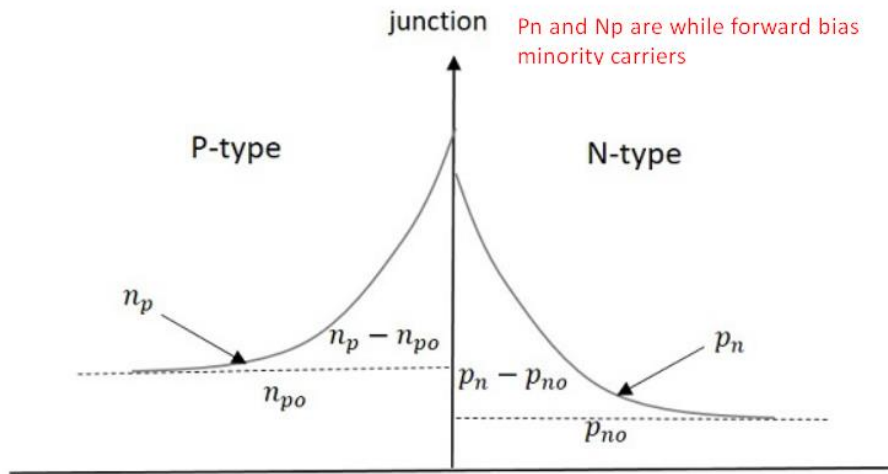


Number of minority carriers increase. So, Excess minority carrier charge in P-type = $p_n - p_{no}$ with p_{no} steady state value, Excess minority carrier charge in N-type = $n_p - n_{po}$ with n_{po} steady state value

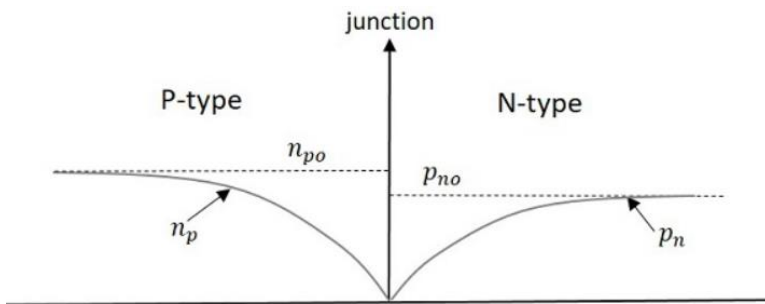Then after giving **Reverse bias**, opposite happens:



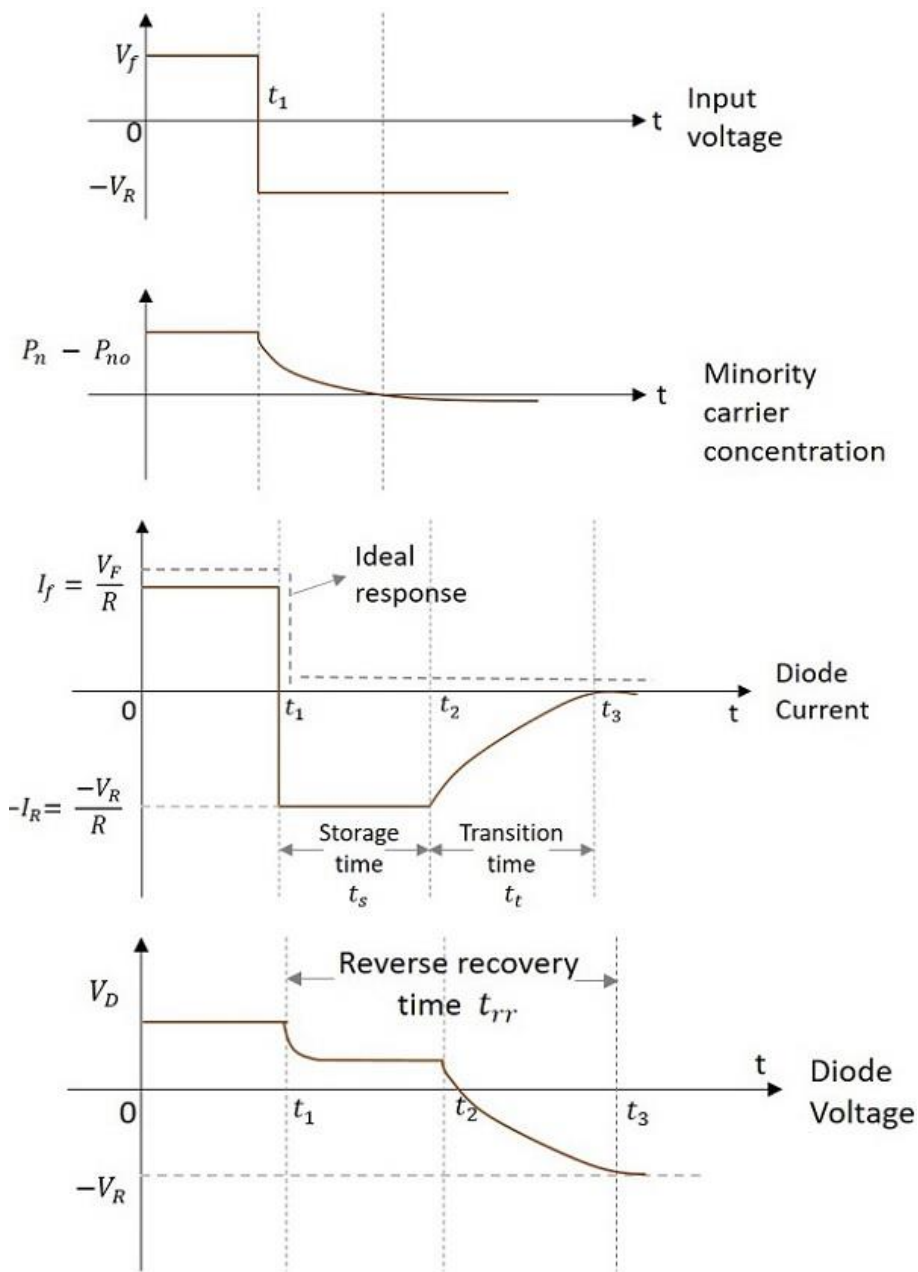As the current due to minority charge carriers is large enough to conduct, the circuit will be ON until this excess charge is removed.



In minority carrier concentration graph, because of the excess minority charge, diode doesn't immediately turn off.

So for diode current, ideal would be zero current immediately, but instead goes negative. For storage time.


Diode voltage goes to negative infinity to become an open circuit, but needs Reverse recovery time which is storage time + transition time.

Storage time – The time period for which the diode remains in the conduction state even in the reverse biased state, is called as Storage time.

Transition time – The time elapsed in returning back to the state of non-conduction, i.e. steady state reverse bias, is called Transition time.


Reverse recovery time – The time required for the diode to change from forward bias to reverse bias is called as Reverse recovery time.

Transistor as switching device:

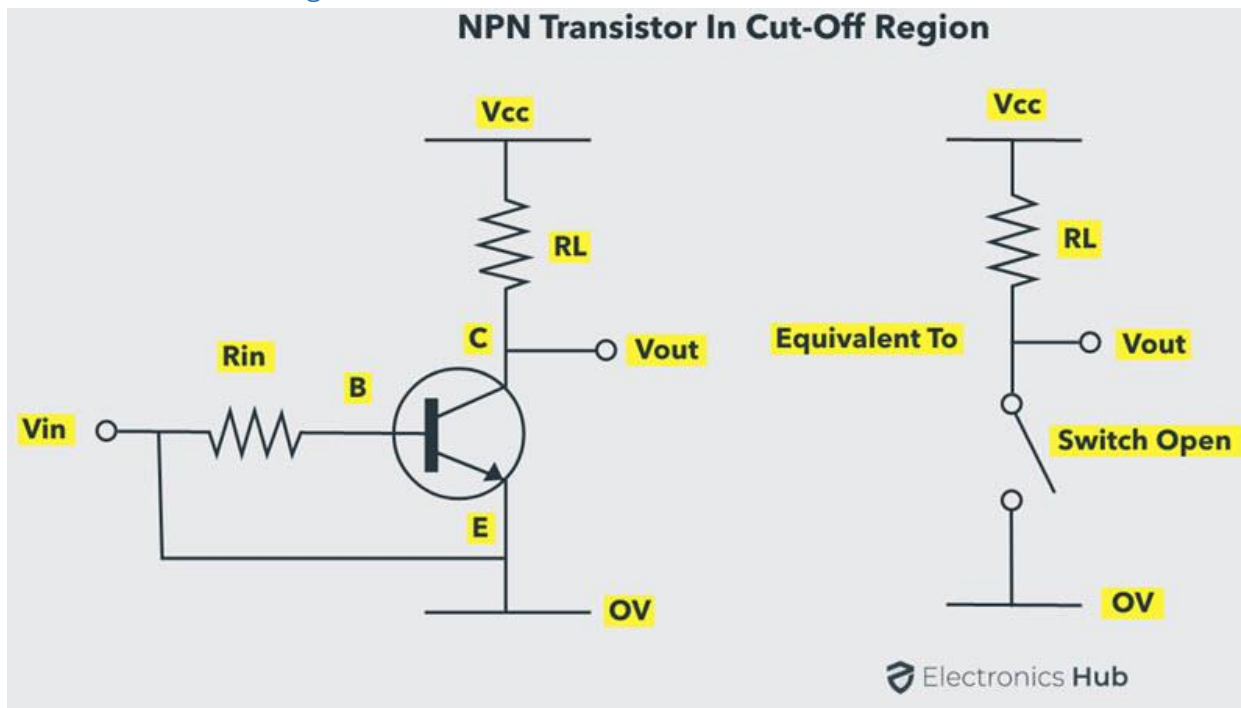

Here, I_c or collector current is zero. $V_{cc} = V_{ce}$

Both P-N junctions are reverse biased.

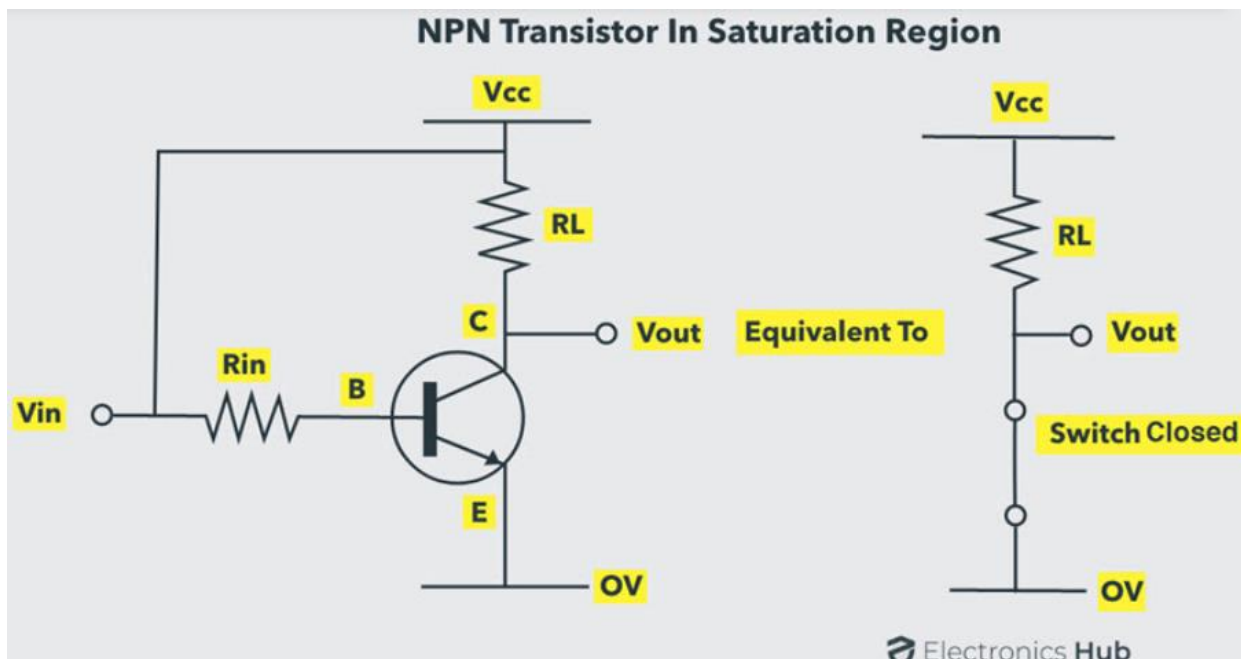

Here, $I_c = V_{cc}/R_c$

Both P-N junctions are forward biased.


OP-AMP as comparator:

OP-AMP Usages:

1. Amplification
2. Math operation

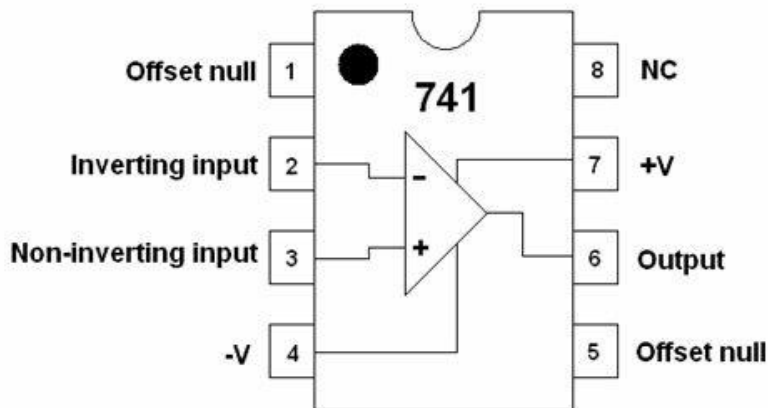
3. Signal shaping (Comparator)

Named OP-AMP from OP(mathematical operation) – AMP(amplification)



-V and +V are biasing voltage

Characteristic curve:

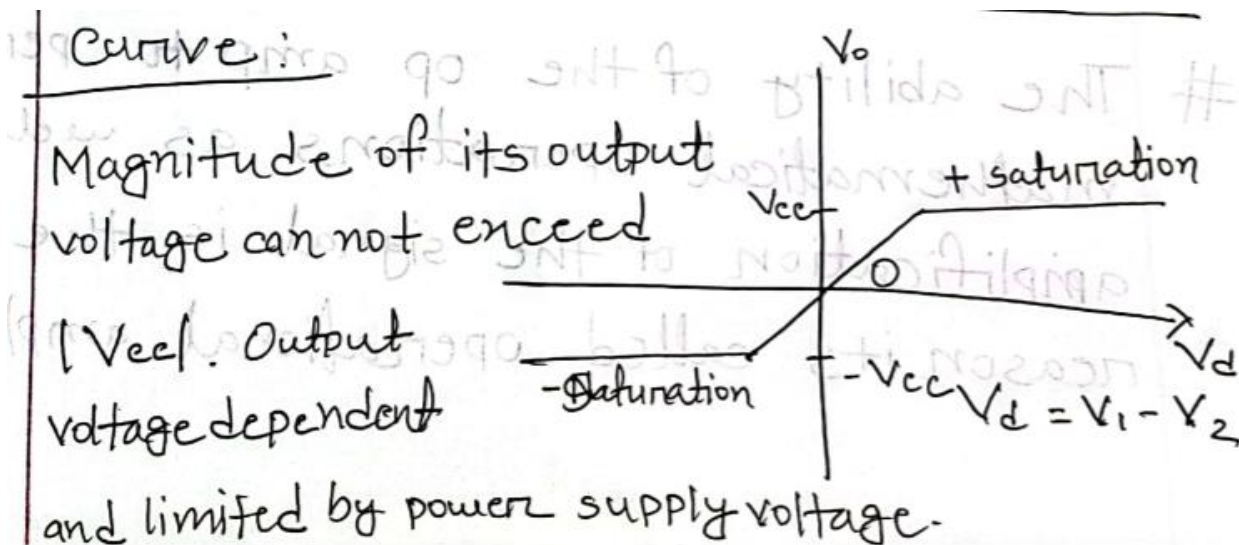


Comparator:

Basically, Output is High/Low if input is higher than a reference voltage, and Low/High if lower than reference voltage. (Non-inverting/ Inverting)


Comparator cause compares with reference voltage.

Comparator is used to generate square or pulse waves.



Comparator reference voltage methods:

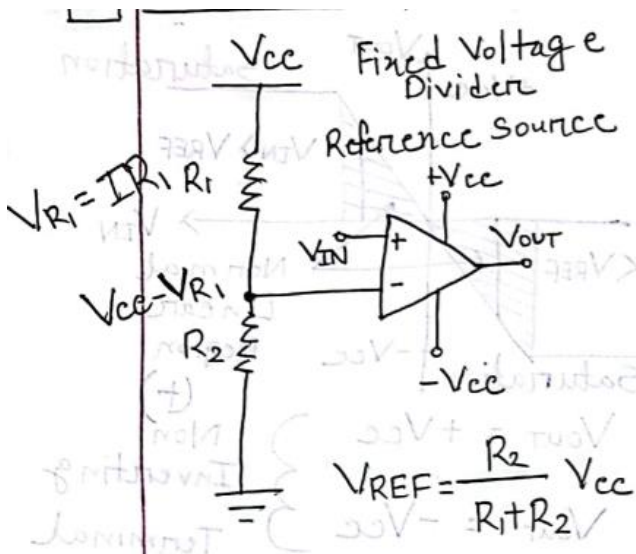

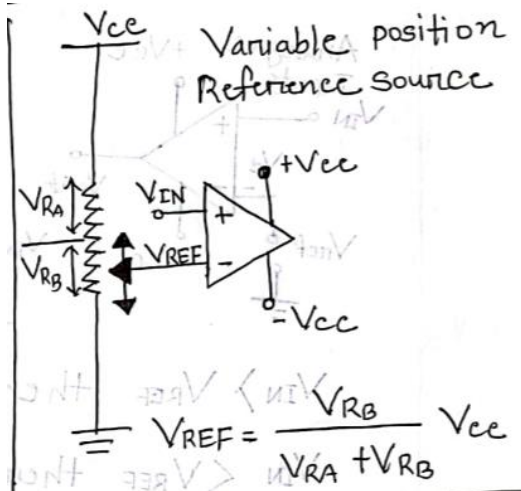
R1 and R2 are controlled to give proper reference voltage as input.



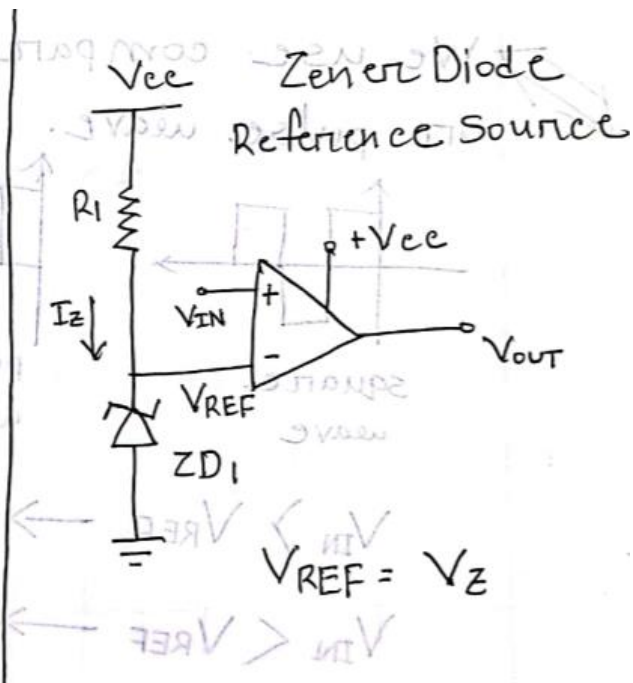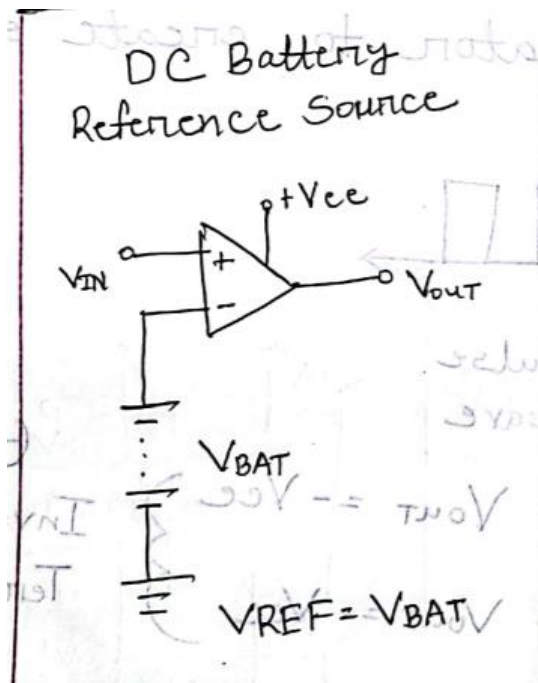Variable resistor for proper reference voltage.





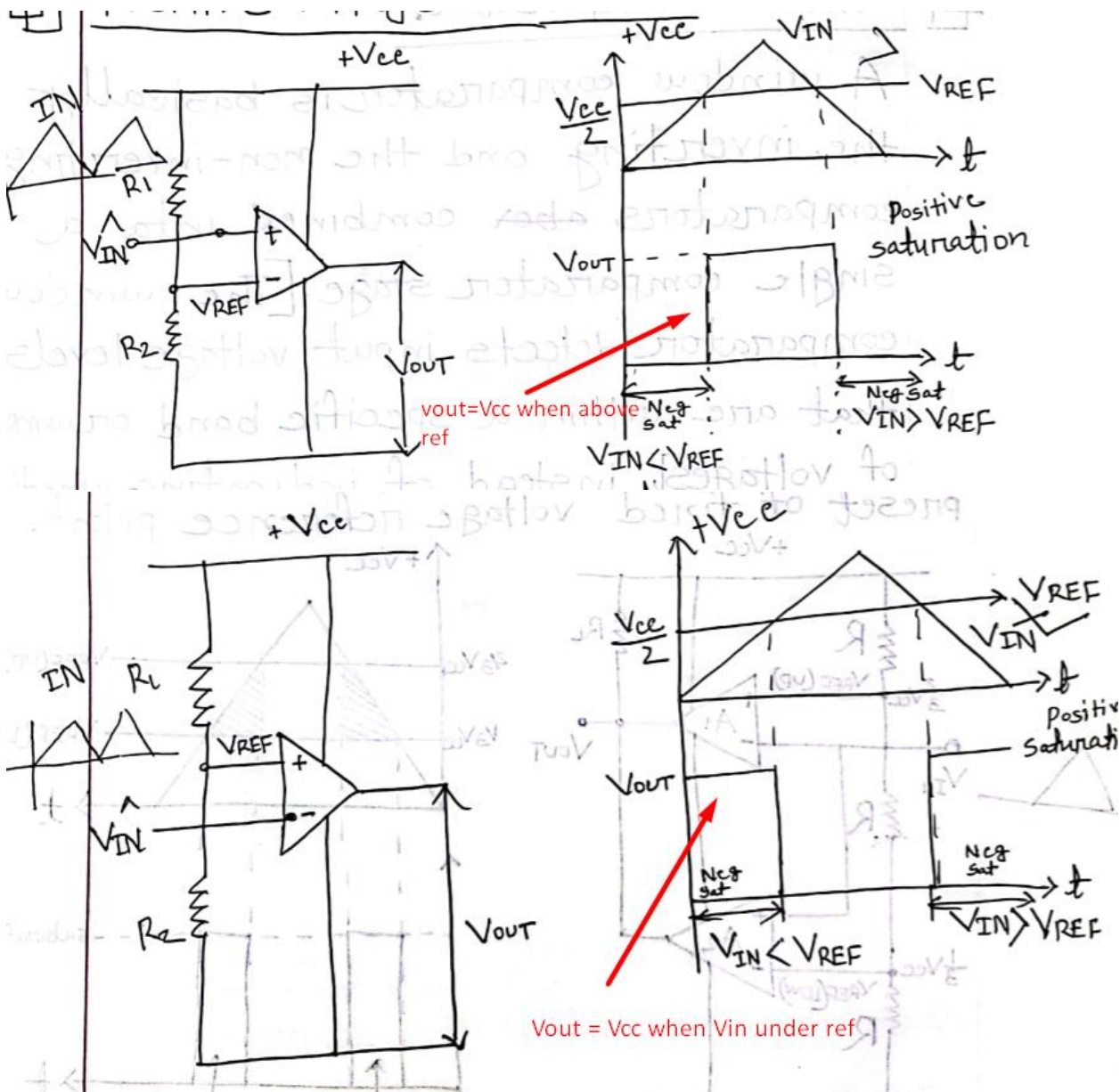Positive and negative voltage comparator:



Window comparator:

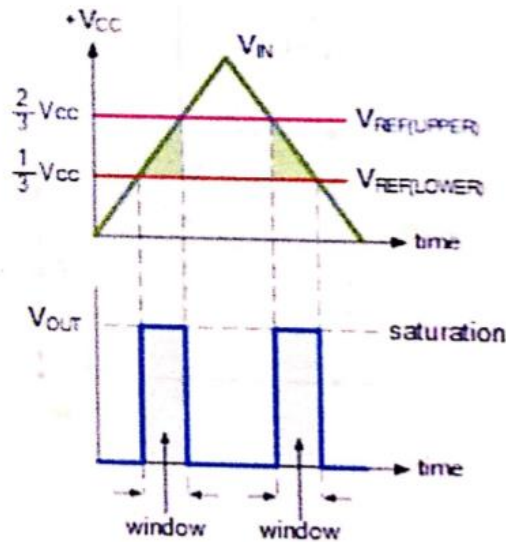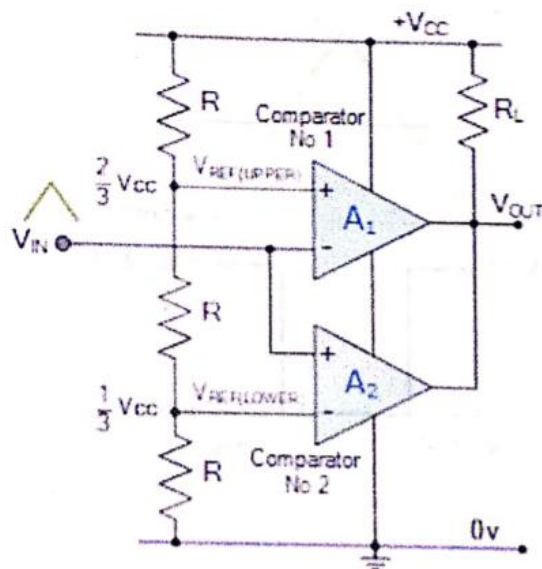Window comparator is when two comparators, one negative and one positive comparator is used to detect voltage input within a window of voltages.



Negative Comparator (Comparator 1)

$V_{IN} < V_{REF} \implies V_{OUT} = \text{Positive Saturation}$


$V_{IN} > V_{REF} \implies V_{OUT} = \text{Negative Saturation}$

Positive Comparator (Comparator 2)

$V_{IN} > V_{REF} \implies V_{OUT} = \text{Positive Saturation}$

$V_{IN} < V_{REF} \implies V_{OUT} = \text{Negative Saturation}$


Problem with OP-AMP comparator:

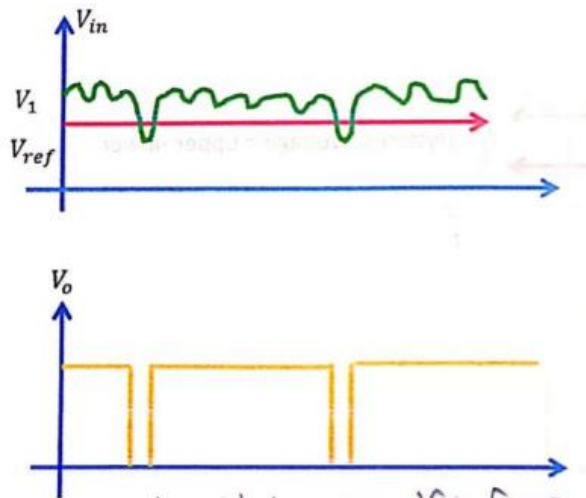


Because of noise, OP-AMP can sometimes get false triggered, creating problems. To solve this, something with a threshold for noise should be used, like Schmitt trigger.

Transfer characteristics graph:

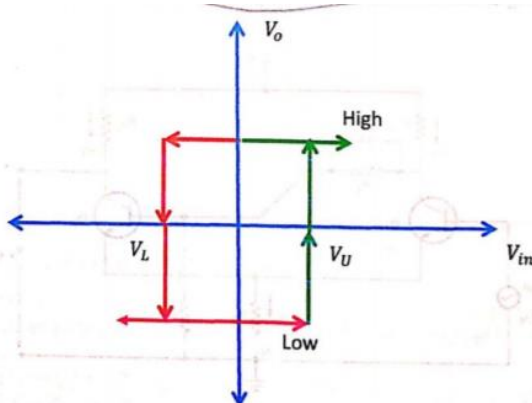When V_{in} is lower than V_{low} , V_o is low, then when V_{in} is higher than V_{up} , V_o is high. For inverting, its just reversed.




This is non-inverting Schmitt Trigger

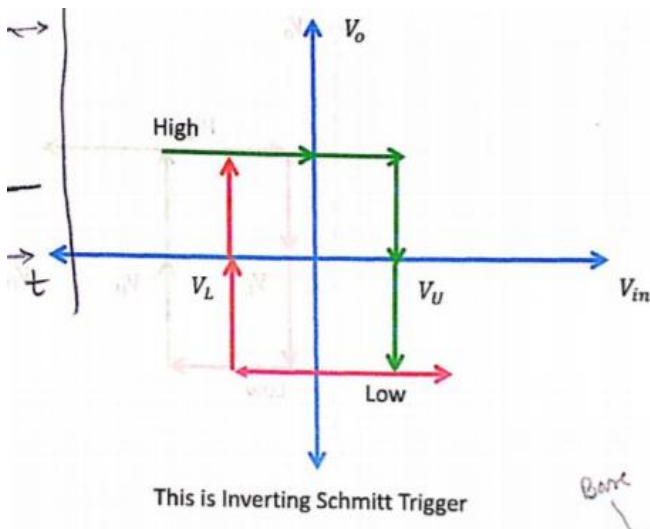

Schmitt trigger using transistors:

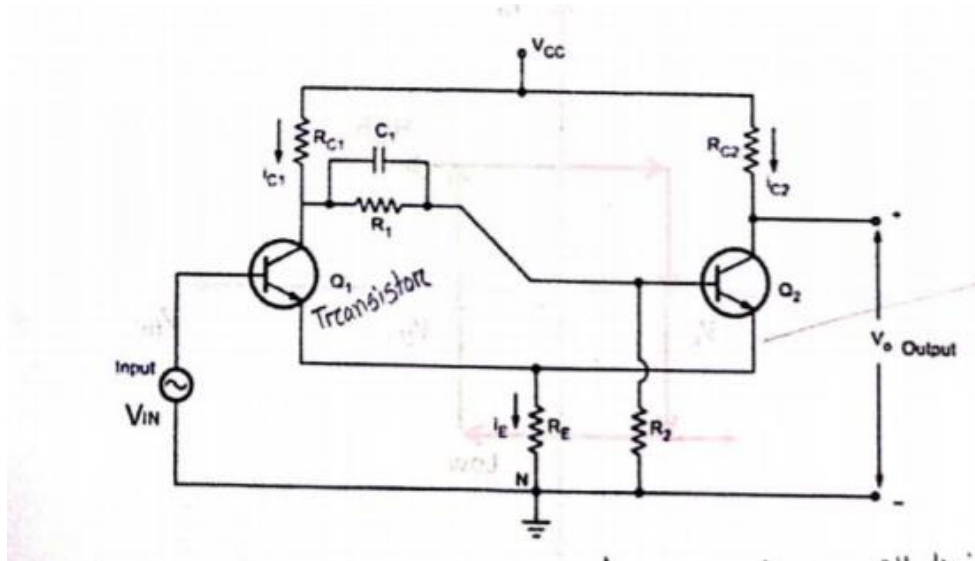Schmitt triggers work like window comparator by providing upper and lower thresholds before counting input as a trigger.



- When V_{in} is zero, V_{cc} turns on Q_2 , so Q_2 is saturated thus works as short circuit, thus V_o being low or zero.
- There is a voltage across R_E through the $R_{C2} \rightarrow R_E \rightarrow$ ground path. It is denoted by,

$$V_{RE} = I \cdot R_E = \frac{V_{CC}}{(R_{C2} + R_E)} \times R_E$$

transistors

- Which is also the emitter voltage of Q_1 , so to turn on Q_1 , V_{in} should be $V_{RE} + 0.7$
- When V_{in} turns on Q_1 , as long the voltage is higher, output is high. The V_{RE} has a new value now,

$$V_{IN} = (V_{CC} \times R_E) / (R_E + R_{C1}) + 0.7$$


This is how it works, the lower threshold and upper threshold is denoted by,

$$V_{LT} = (V_{CC} \times R_E) / (R_E + R_{C1}) + 0.7$$

$$V_{UT} = (V_{CC} \times R_E) / (R_E + R_{C2}) + 0.7$$

OP-AMP based Schmitt trigger:

Inverting Schmitt trigger circuit:

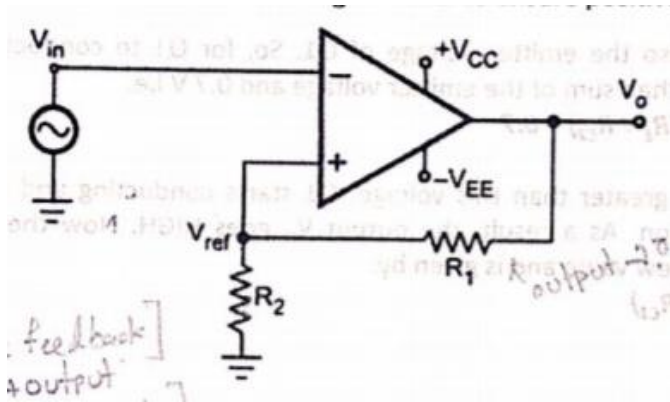

$$V_{REF} = (V_{SAT} \times R2) / (R1 + R2)$$


$$-V_{REF} = (-V_{SAT} \times R2) / (R1 + R2)$$

1. A threshold is introduced by using the Vo as a positive feedback.
2. Vo is either +Vcc or -Vcc. That is taken and then controlled using R1 and R2 to use as Vref.
3. When +Vcc is Vo, it is upper threshold and vice versa.

Non inverting Schmitt trigger:

Non-Inverting Schmitt Trigger Circuit

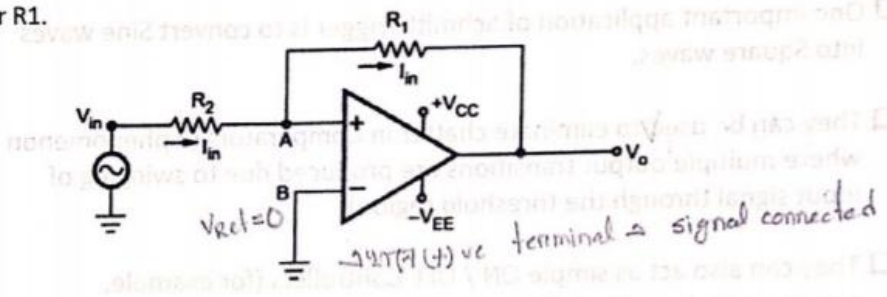
Coming to Non-Inverting Schmitt Trigger, the input in this case is applied to the non-inverting terminal of the Op-Amp. The output voltage is fed back to the non-inverting terminal through the resistor R1.



Let us assume that initially, the output voltage is at V_{SAT} . Until V_{IN} becomes less than V_{LT} , the output stays at this saturation level. Once the input voltage crosses the lower threshold voltage level, the output changes state to $-V_{SAT}$.

The output remains at this state until the input rises beyond the upper threshold voltage.

OUTPUT WAVES:

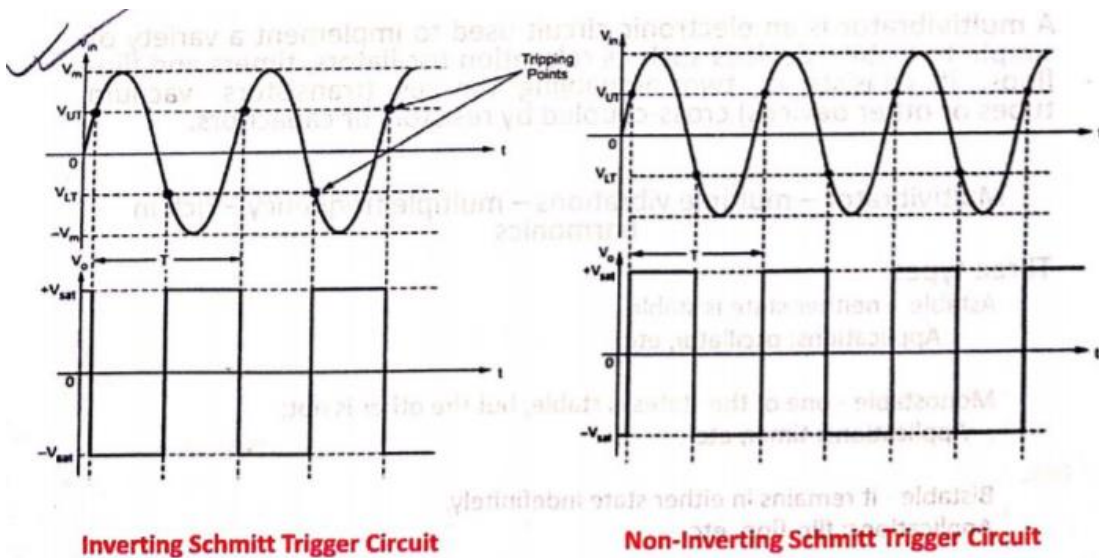


Multi-Vibrator:

A multivibrator is an IC that is used to create different two state devices. It consists two amplifying devices that are cross coupled.

Three types:

1. Astable – Oscillator
2. Monostable – Timer
3. Bistable – flipflop


Waveshapes:

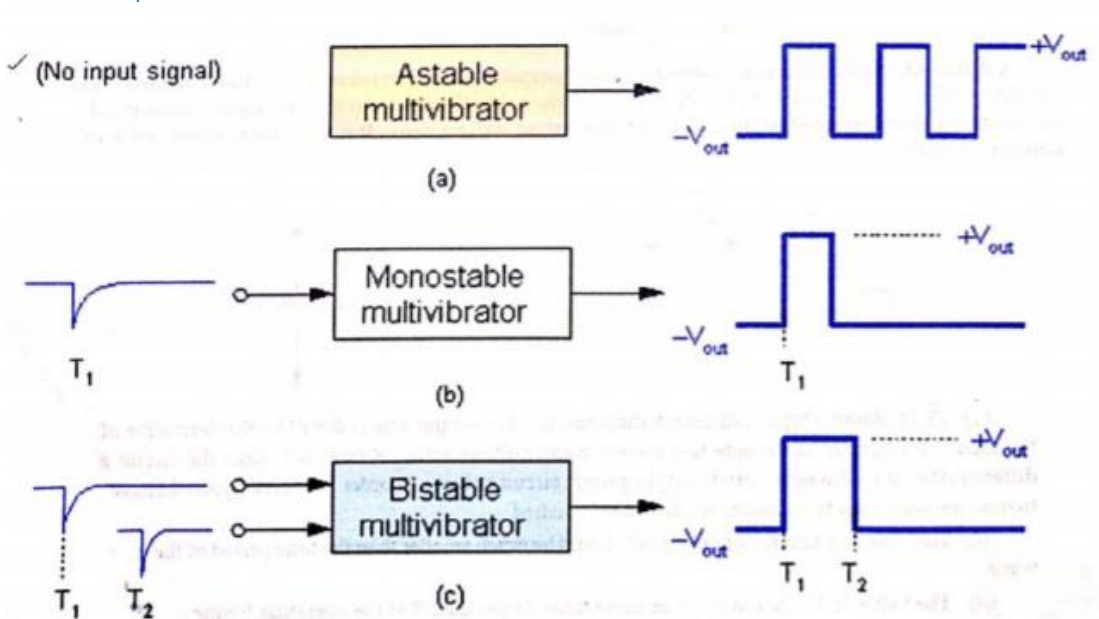

Trigger pulse generation:

A circuit where the output is derivative of the input

$$V_o = d/dt(V_{in})$$

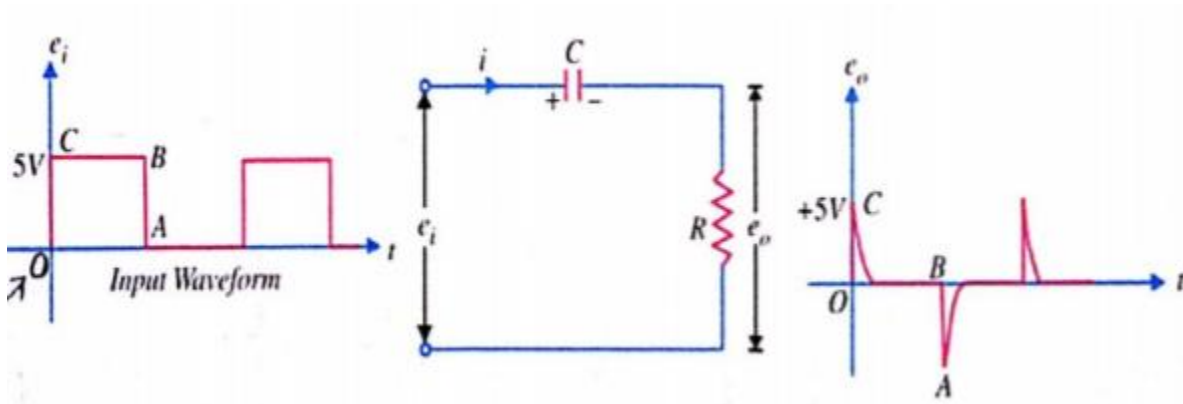


Requirements:

1. RC circuit time constant $.69RC$ should be much smaller than input wave period.
2. Capacitive resistance should be 10 or more times higher than R .


Bistable:

What is Bistable Multivibrator

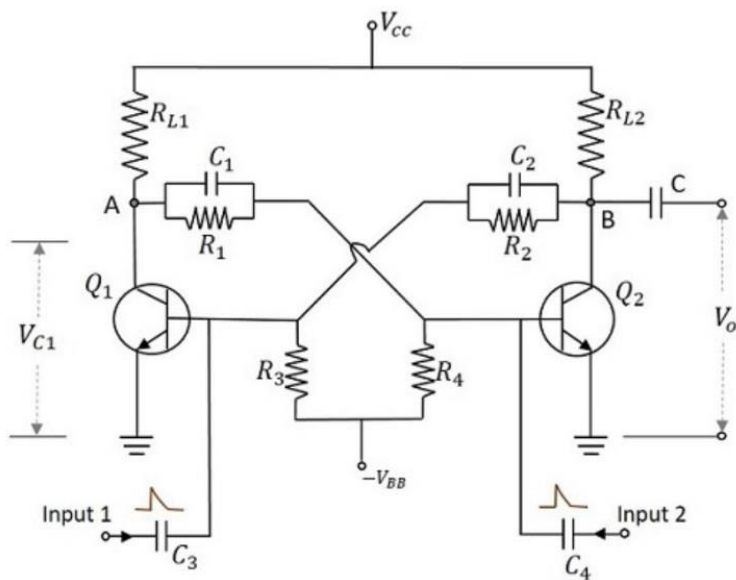

1. When turned on, one of either of the transistors are on, let's say Q_2 .
2. When given trigger to Q_1 , collector current of Q_1 is quickly increased, and collector voltage decreases.
3. Which is applied to the Q_2 base, thus decreasing its collector current and increase base voltage, which is then applied to Q_1 base, thus creating a loop. Eventually collector current of Q_2 is zero and Q_1 is on.

Monostable:

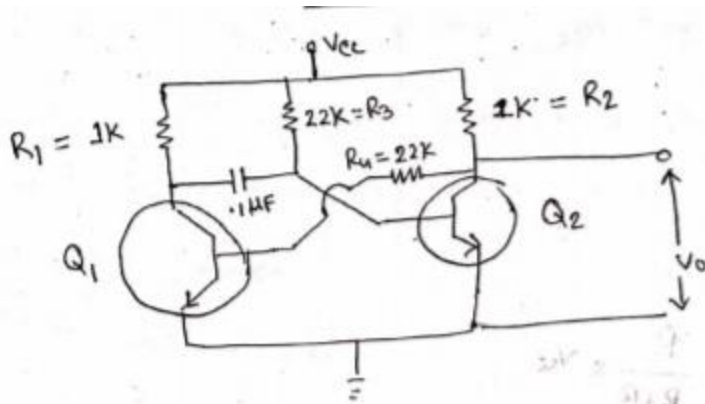

When applied initial V_{cc} , Q_1 is off so goes $R_3 > Q_2$ Base, which is the lowest resistance path.


Q_2 is turned on, so V_{cc} now goes through R_2 to ground. So V_o is low as short circuit. Capacitor is being charged.

When applied trigger, Q_1 is turned on, so V_{cc} goes through R_1 to ground. Q_2 is off. Then after a time capacitor is discharged, turning

on Q_2 , which in result turns off Q_1 . Q_2 is stable state transistor.

Astable:

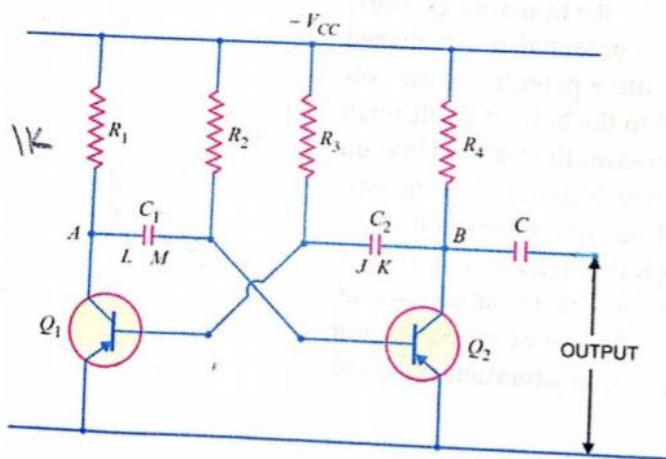It is the non-stable part of Monostable x2. Doesn't need any trigger to switch state.



V_{cc} first turns on either, let say Q_1 .

C_1 is being charged. After some time, C_1 discharges, turning on Q_2 and starting charging of C_2 .

The on off time is determined by RC constant.

ON or OFF time. The time for which either transistor remains ON or OFF is given by :

ON time for Q_1 (or OFF time for Q_2) is

$$T_1 = 0.694 R_2 C_1$$

OFF time for Q_1 (or ON time for Q_2) is

$$T_2 = 0.694 R_3 C_2$$

Total time period of the square wave is

$$T = T_1 + T_2 = 0.694 (R_2 C_1 + R_3 C_2)$$

As $R_2 = R_3 = R$ and $C_1 = C_2 = C$,

$$\therefore T = 0.694 (RC + RC) \approx 1.4 RC \text{ seconds}$$

Frequency of the square wave is

$$f = \frac{1}{T} \approx \frac{0.7}{RC} \text{ Hz}$$